

Lab 2: Basic Circuits

SUMMER CHALLENGE COURSE SMART LIGHTING

Ayse Coskun

ECE Department

acoskun@bu.edu

Slides by: Hany Elgala, PhD



Solderless Breadboards

numbers & letter labels just for reference

All connected, a "bus"

groups of 5 connected

not connected

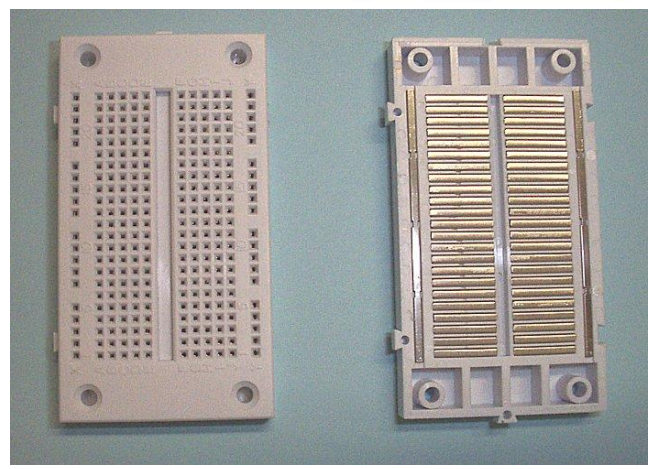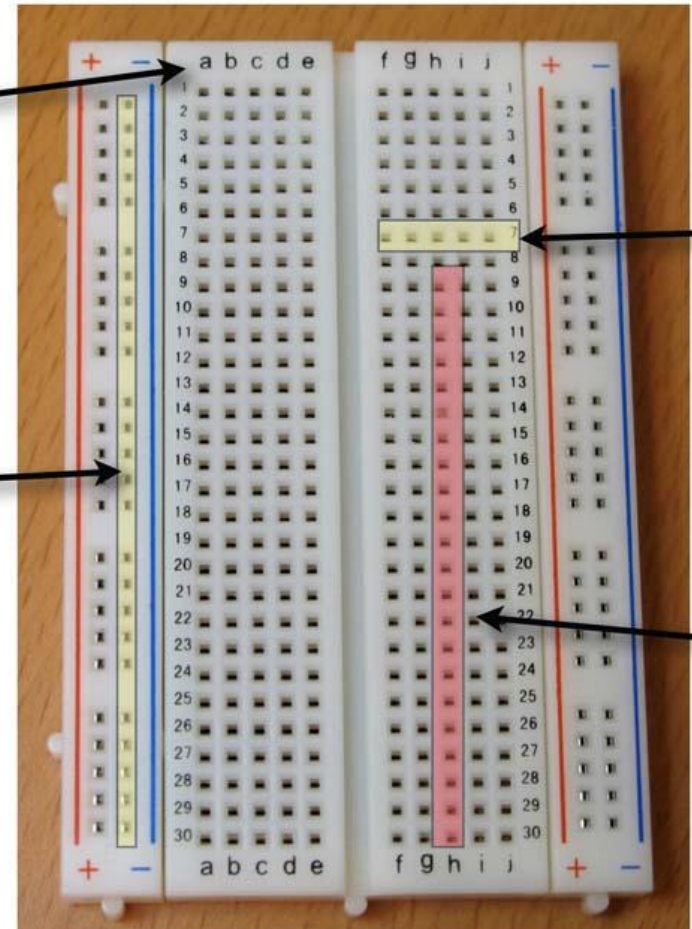

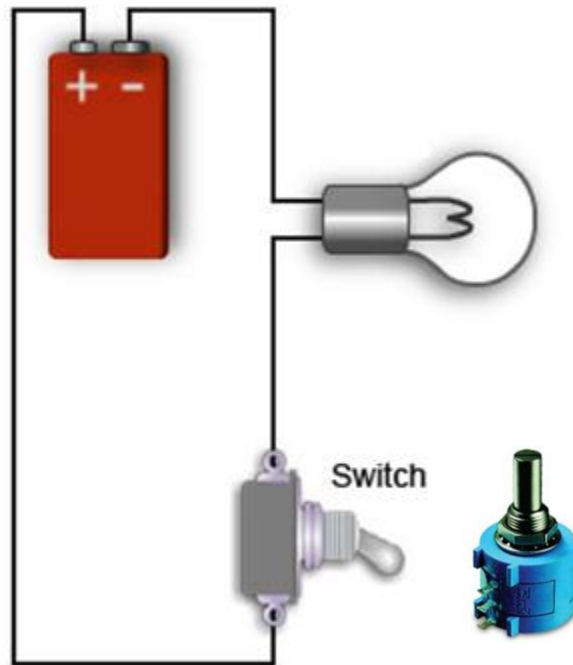


Figure 1: Electrical


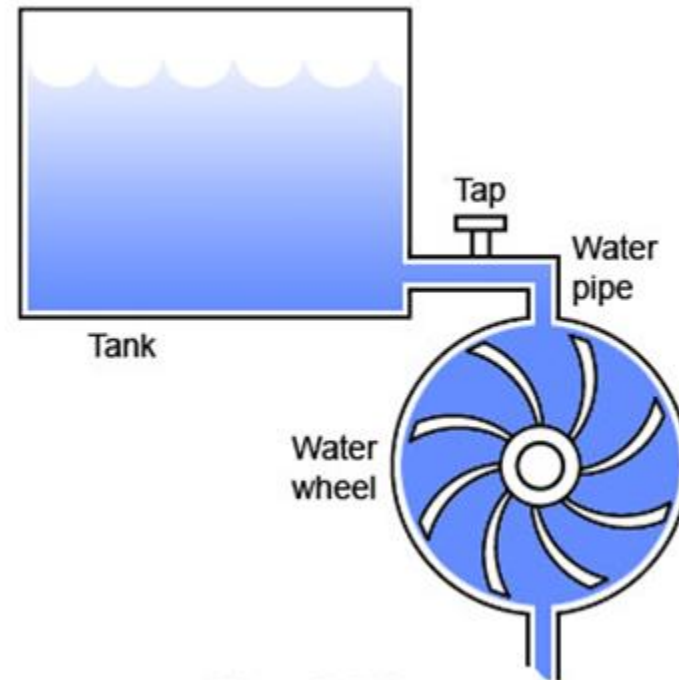
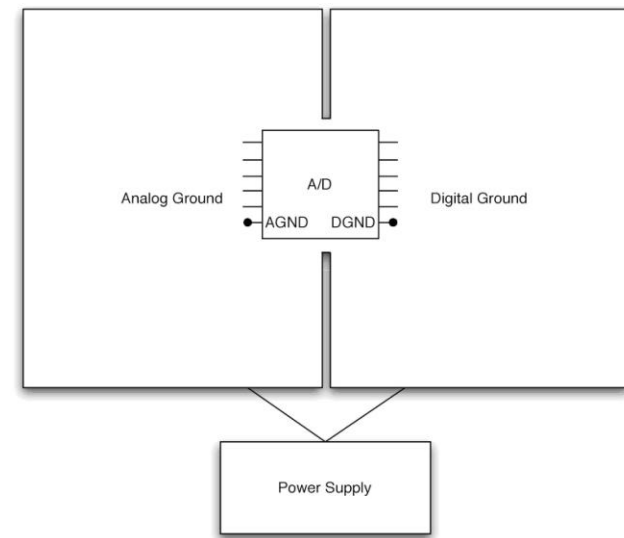


Figure 2: Water

- Water pressure stored in the tank is similar to **voltage** (electrical pressure) stored in a battery.
- The flow of water through a pipe is similar to the flow of **current** through a wire.
- The path the current flows through has a certain amount of **resistance**.

- Ground is a reference point for all of the signals in a system.
- Ideally, it has a potential of zero volts everywhere.
- A "good" ground is realized by keeping the conductor impedance low, which minimizes the potential difference. This is done by dedicating a layer of the printed circuit board to being a ground plane, where a large area of copper lowers the impedance.
- In order to prevent coupling, the AGND and DGND pins should be joined together externally to the same low impedance ground plane; AGND and DGND are not connected inside the data converter IC.

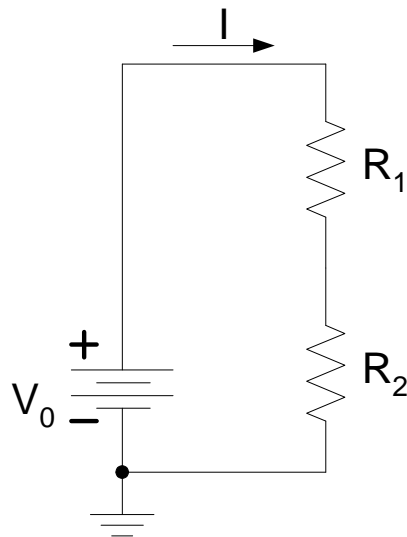

Georg Simon Ohm (1789 – 1854)



Ohm's Law: The voltage across a resistor is directly proportional to the current flowing through it.

German professor who publishes a book in 1827 that includes what is now known as Ohm's law.


$$i = \frac{v}{R} \quad \begin{array}{c} + \quad v \quad - \\ + \circ \rightarrow \text{---} R \text{---} \circ - \end{array} \quad R = \frac{v}{i}$$

Units of resistance, R , is Ohms (Ω)


$R = 0$: short circuit


$R = \infty$: open circuit

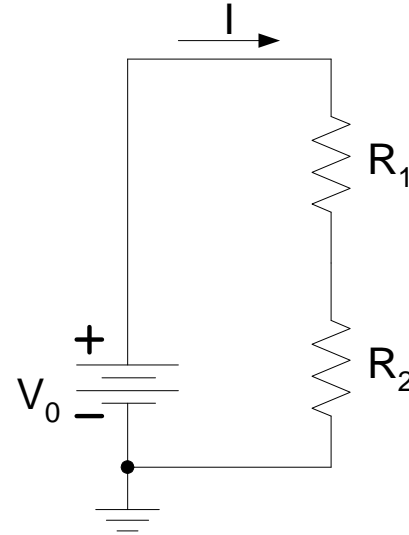Two or more elements are connected in **series** if they carry the same current and are connected sequentially.



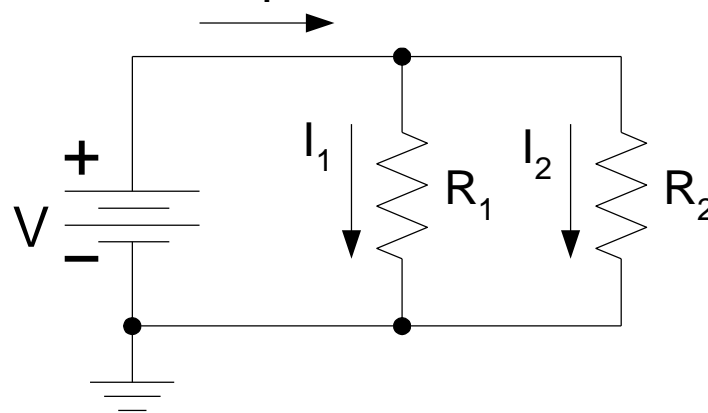Two or more elements are connected in **parallel** if they are connected to the same two nodes & consequently have the same voltage across them.



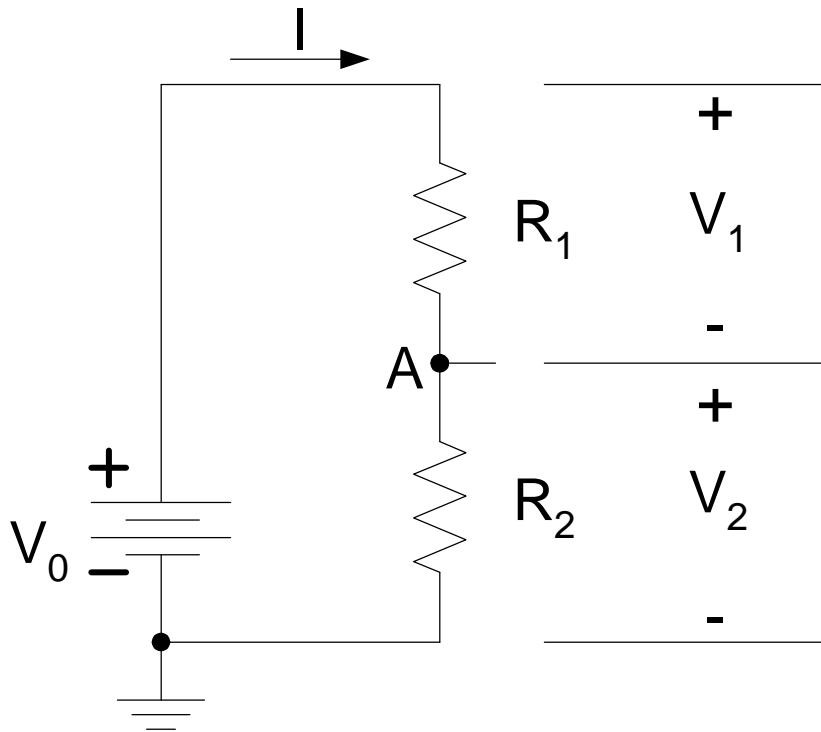



$$V_0 = V_1 + V_2 = IR_1 + IR_2$$

$$= I R_1 + R_2$$

$$= IR_s$$

$$R_s = R_1 + R_2$$

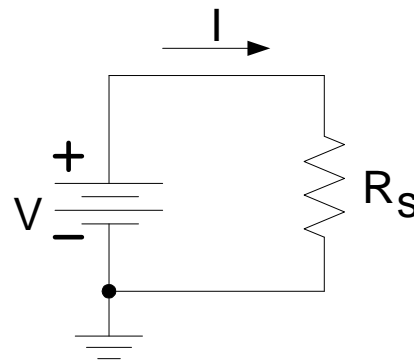

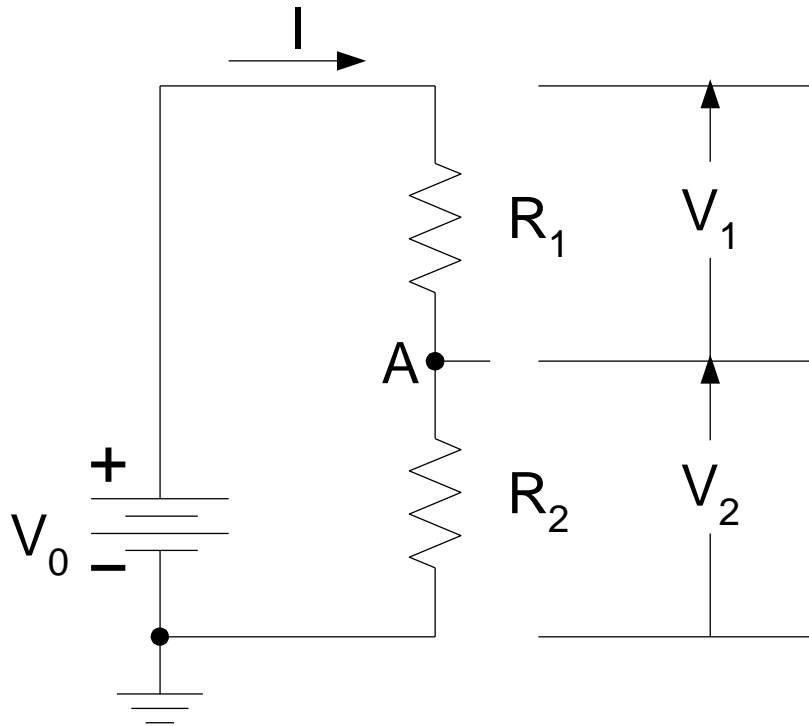


$$I = \frac{V_0}{R_s} = \frac{V_0}{R_1 + R_2}$$

$$V_2 = IR_2 = \frac{V_0}{R_1 + R_2} R_2$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_0$$

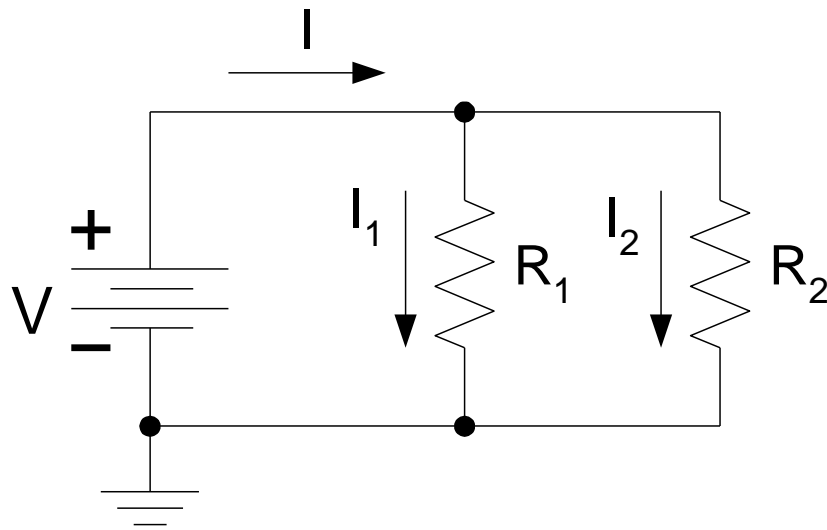
$$\text{Also } V_1 = \frac{R_1}{R_1 + R_2} V_0$$



$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2}$$


$$= V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{V}{R_p}$$

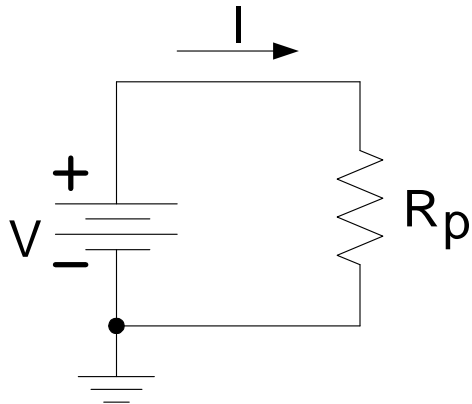

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

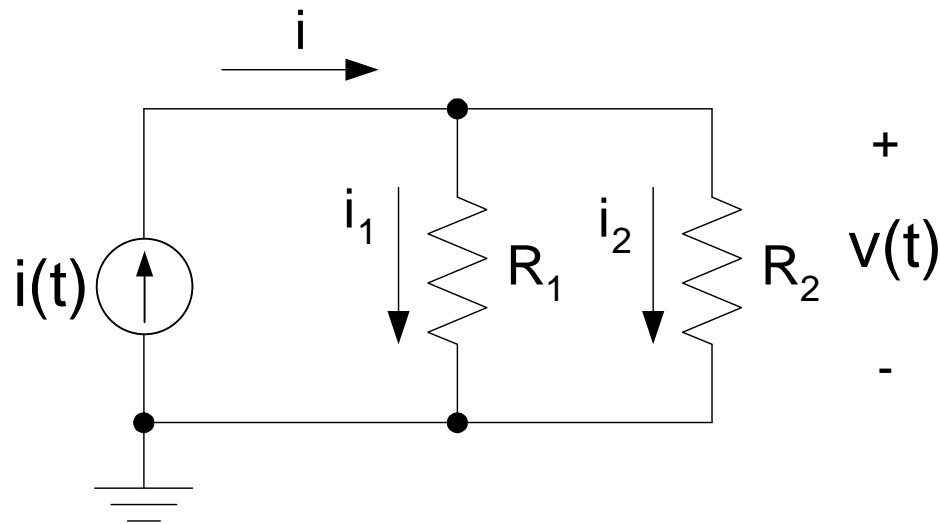


$$i_1(t) = \frac{v(t)}{R_1} = \frac{R_2}{R_1 + R_2} i(t)$$

$$i_2(t) = \frac{v(t)}{R_2} = \frac{R_1}{R_1 + R_2} i(t)$$


$$v(t) = R_p i(t) = \frac{R_1 R_2}{R_1 + R_2} i(t)$$


Current divides in inverse proportion to the resistances

Resistor Color Code

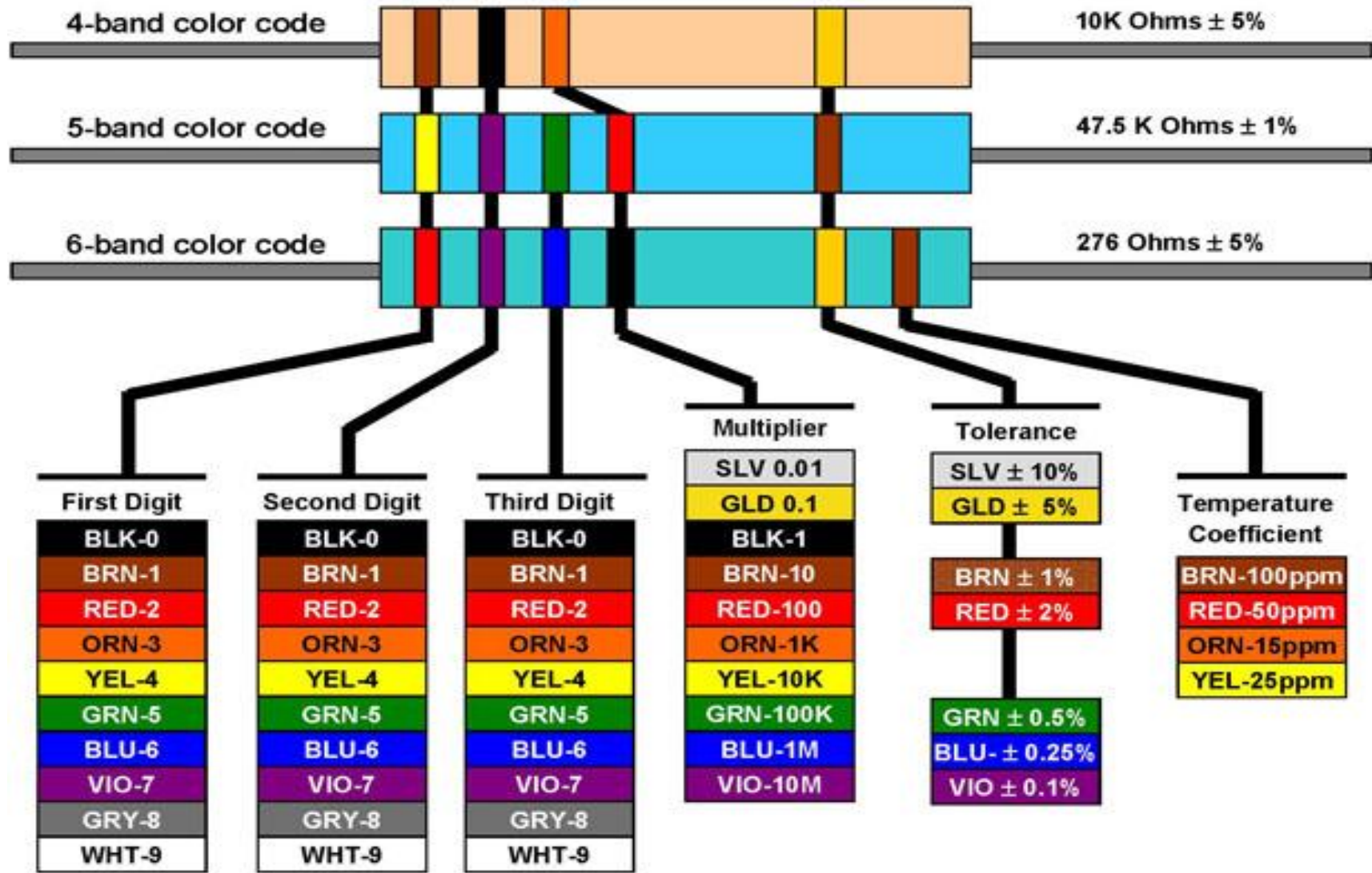


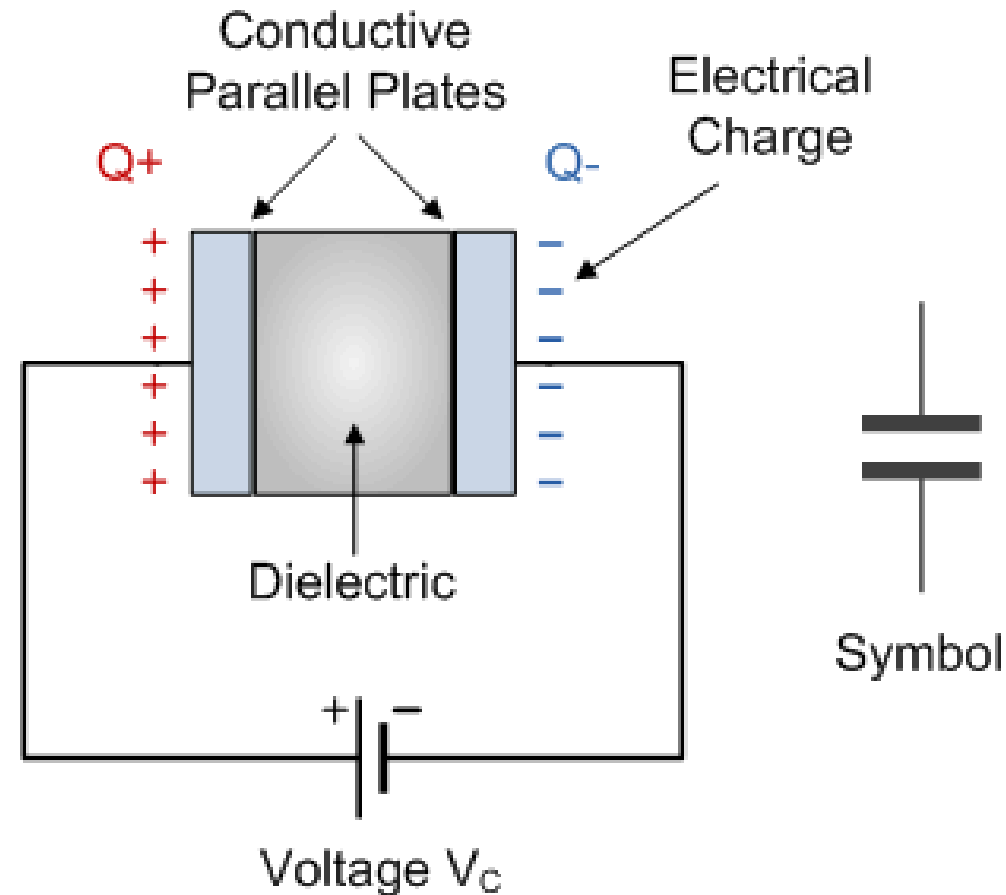
The **capacitor** has the capacity to store energy in the form of an electrical charge producing a voltage across its plates, much like a small rechargeable battery.





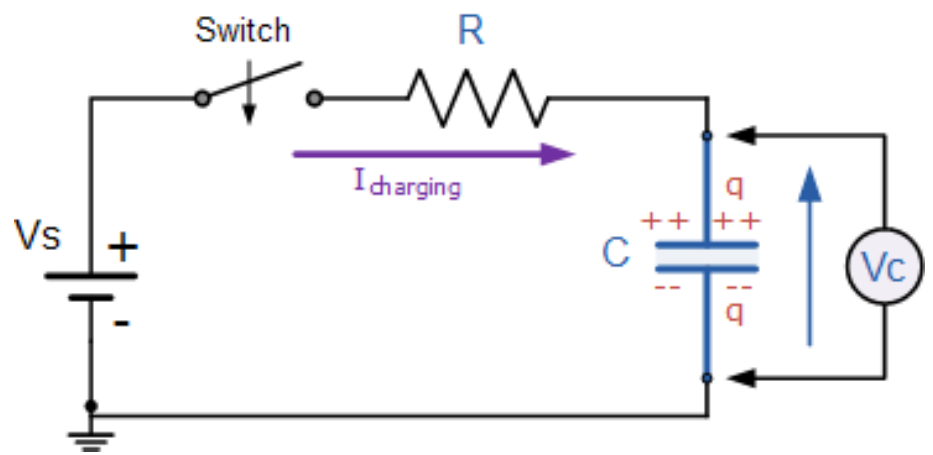

$$\tau \equiv R.C$$

$$V_c = V_s(1 - e^{-t/RC})$$

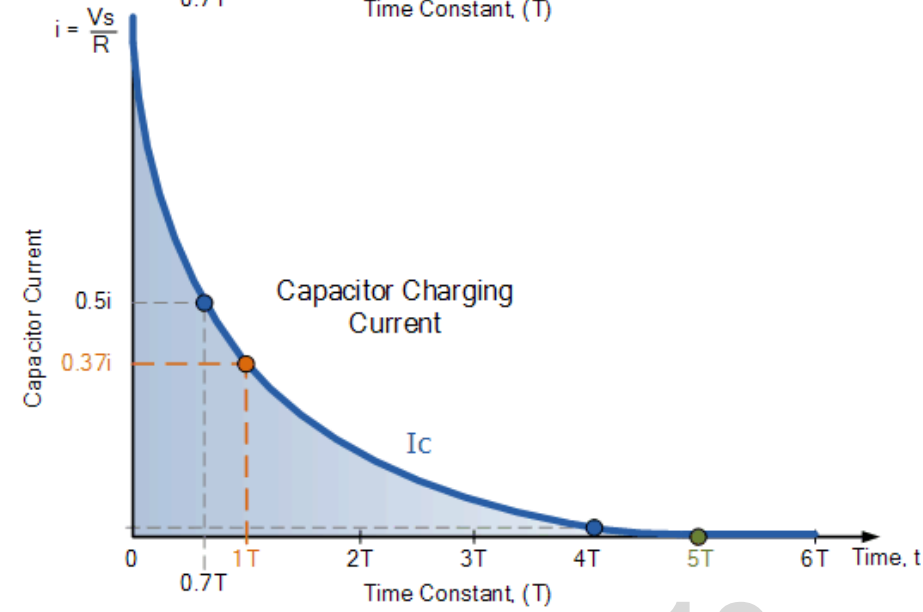
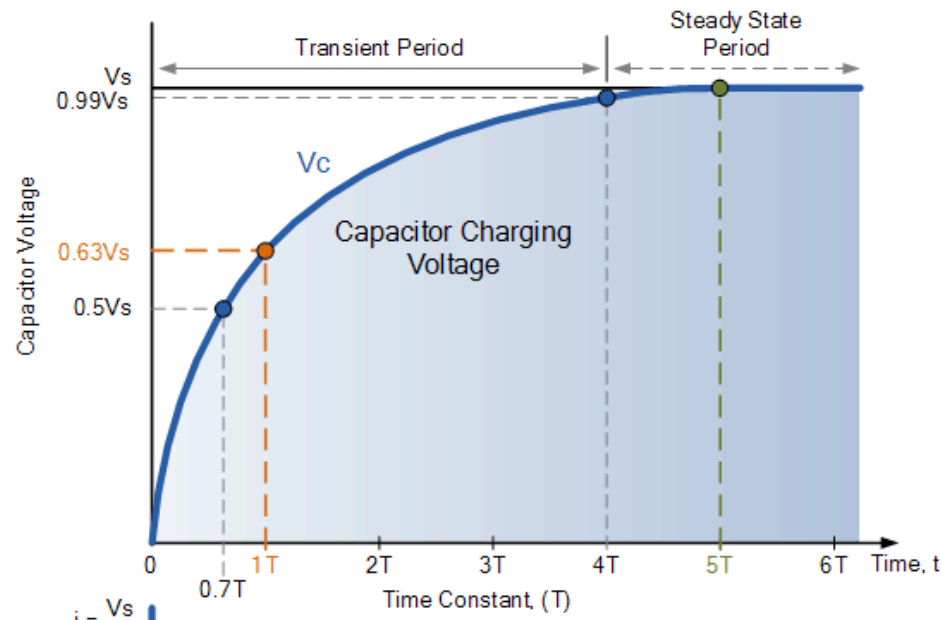


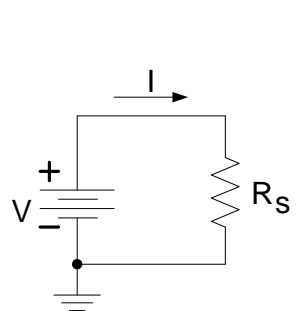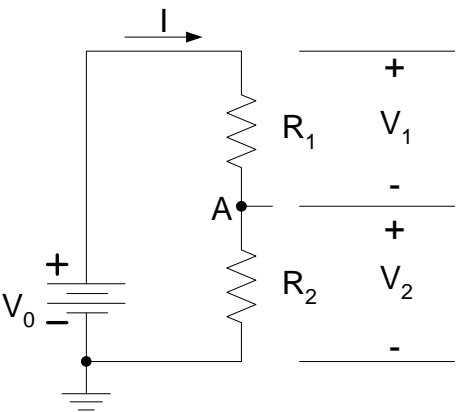

$$V_0 = V_1 + V_2 = IR_1 + IR_2 = I R_1 + R_2 = IR_s$$

$$R_s = R_1 + R_2 \quad I = \frac{V_0}{R_s} = \frac{V_0}{R_1 + R_2}$$

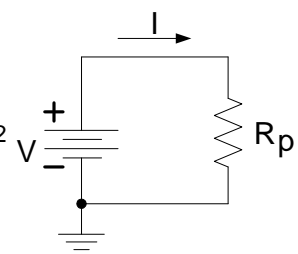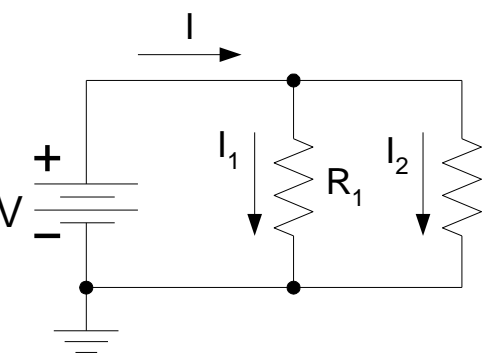Also $V_1 = \frac{R_1}{R_1 + R_2} V_0$ $V_2 = \frac{R_2}{R_1 + R_2} V_0$



$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \quad R_p = \frac{R_1 R_2}{R_1 + R_2} \quad V = R_p I = \frac{R_1 R_2}{R_1 + R_2} I$$

$$I_1 = \frac{V}{R_1} = \frac{R_2}{R_1 + R_2} I \quad I_2 = \frac{V}{R_2} = \frac{R_1}{R_1 + R_2} I$$