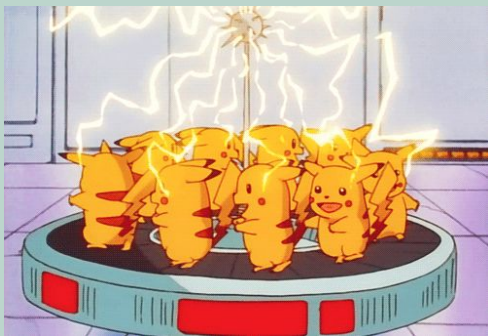


Electricity and Circuits

By Jocelyn Pern, Shakaani Nasankar,
and Danielle Aguiar



Electricity



I don't get electricity jokes. Watts so funny about them?

“... the set of physical phenomena associated with the presence and motion of electric charge”
(Wikipedia)


In other words...

A form of energy caused by charged particles

What does a light bulb eat for fresh breath?

The Energy Theory

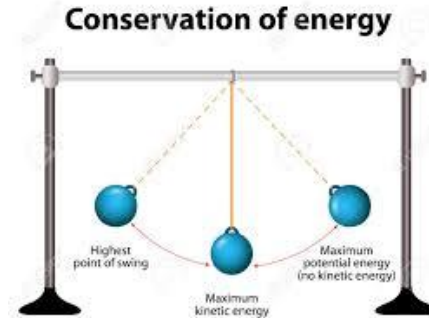The Conservation of Energy states that energy cannot be created or destroyed, only altered from one form to another.



Fila-mint!




Positive vs. Negative Charge

Static vs. Dynamic


Positive charge = lose electrons

Negative charge = gain electrons

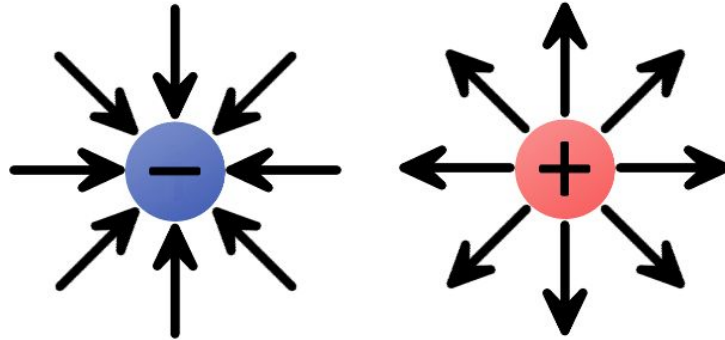

Static - particles stay together

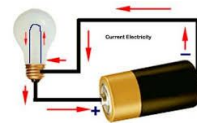
Dynamic - particles move in same direction



Voltage


VS.

Current

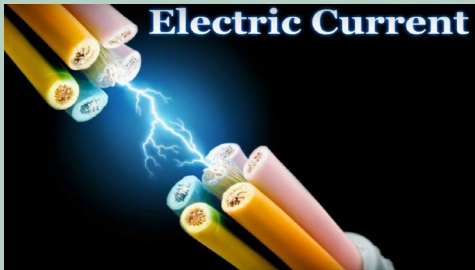


voltage - measure of energy between two points

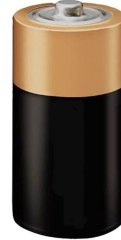- supplied by a battery/power supply
- measured in Volts (V)
- can be measured using a voltmeter




VOLTAGE

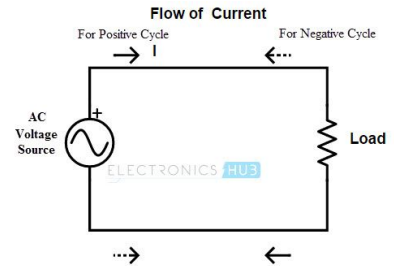

current - direction of the flow of charged particles


- flows from positive to negative potentials
- measured in Ampere (amp)

Direct and Alternating Currents

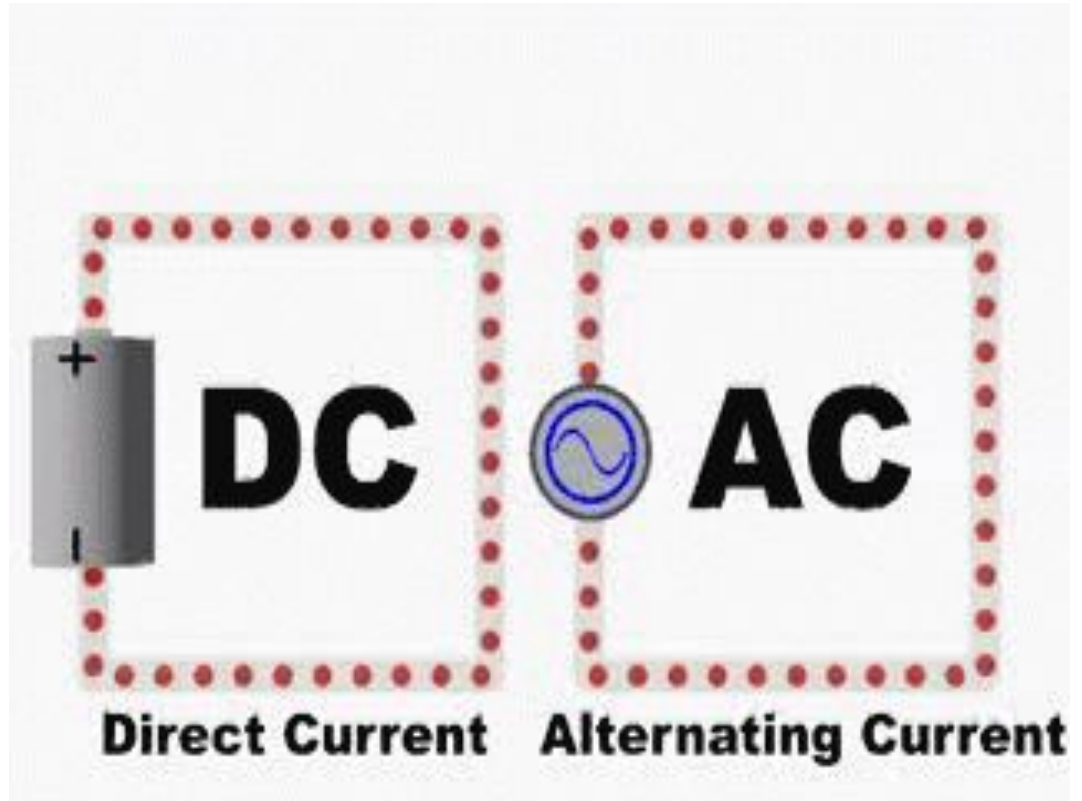

What's an electrician's favorite ice cream flavor?

Circuits

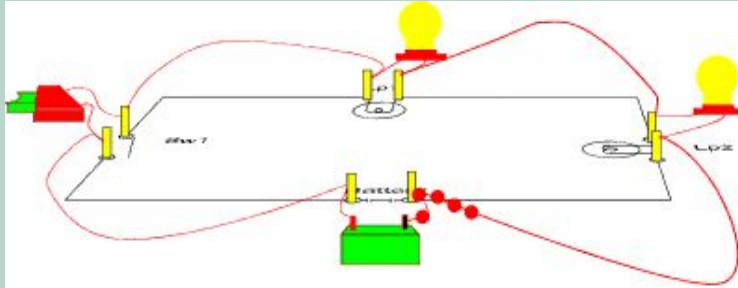


circuit- a closed path where electricity flows
where a battery is energy source




Shock-a-late

Schematic Diagram

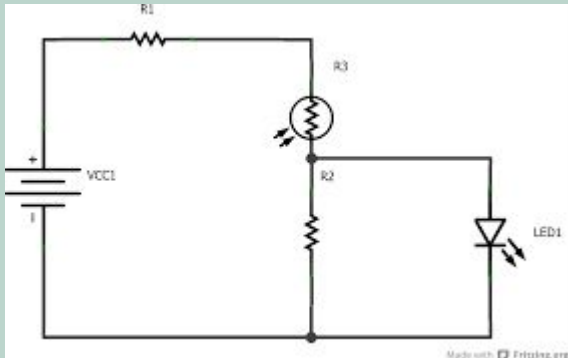

- shows the layout of a circuit
- uses symbols for the electrical components instead of realistic pictures
- shows current, voltage, and resistance
 - I = current
 - V = voltage
 - R = resistance

Circuit Components

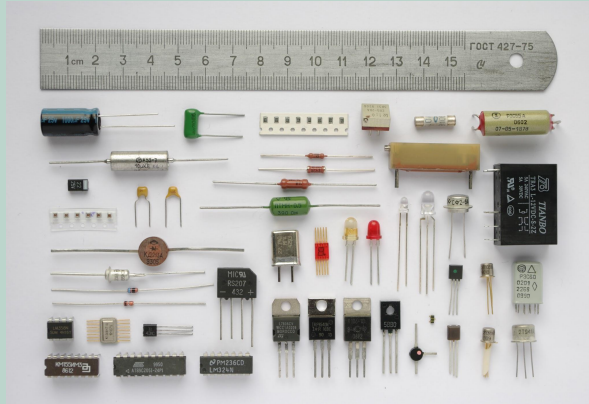

- parts of a circuit
- loads (such as resistors, capacitors, and inductors)

Resistors



4-Band-Code

2%, 5%, 10% 560k Ω \pm 5%


COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black		0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)

5-Band-Code

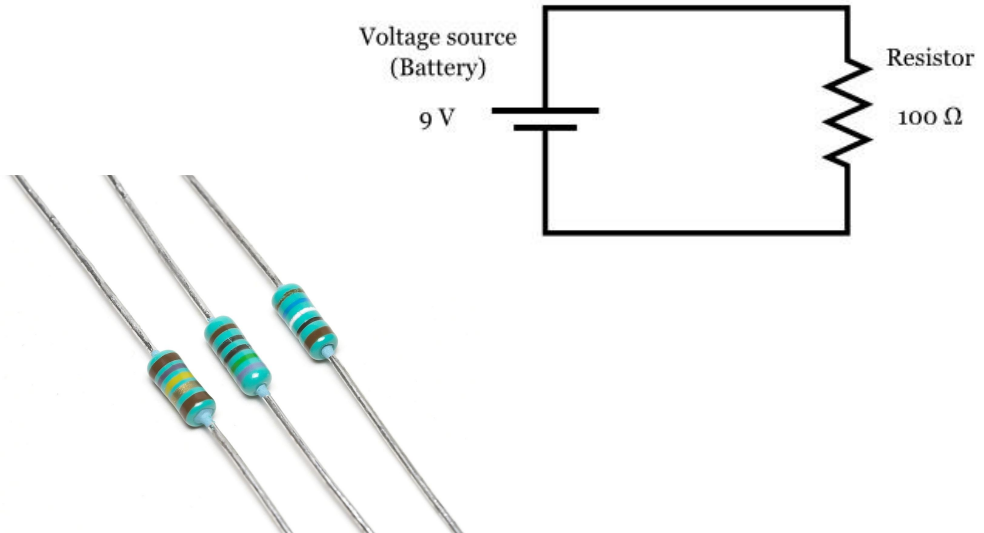
0.1%, 0.25%, 0.5%, 1% 237 Ω \pm 1%

resistors - controls the current flowing through a circuit

- ❑ less resistance = more current
- ❑ measured in Ohms (Ω)
- ❑ Related to Ohm's Law ($V=IR$)
- ❑ color strips around resistor tell the amount of resistance





Capacitors

 


capacitors - two charged plates (positive and negative) that resist sudden shifts in the Voltage

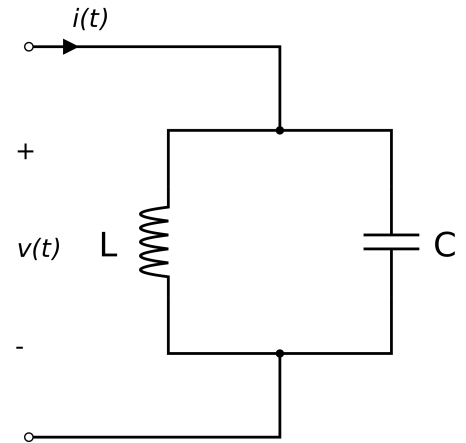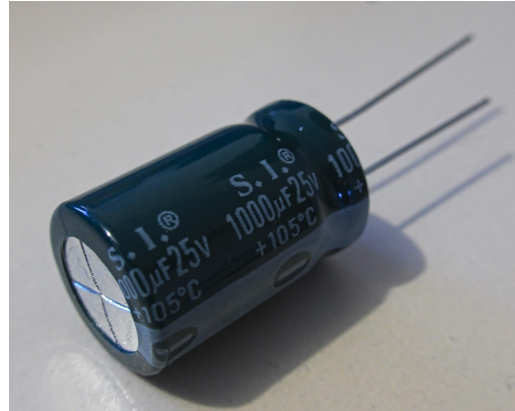
- ❑ when fully charged, the current stops because it becomes an open circuit
- ❑ stores energy in an electric field



Inductors

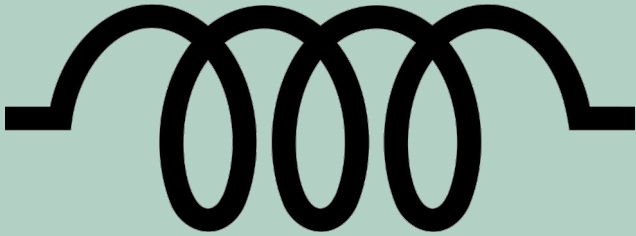

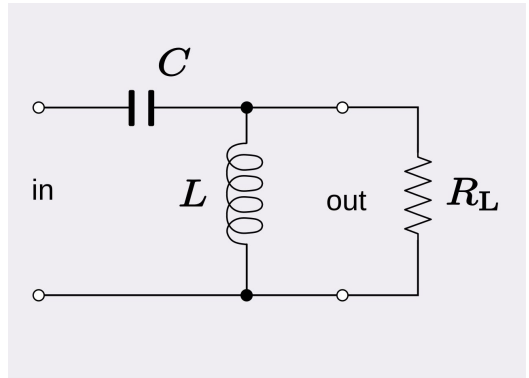
inductors - a coil that stores energy in the form of a magnetic field and resists sudden changes in the current



Switches

switch- a component that opens and closes

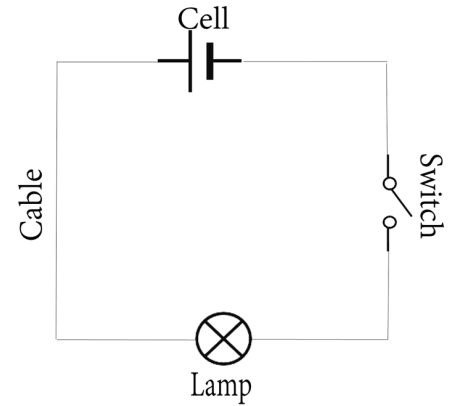- can be used to open and close a circuit
- light switch- when you turn the light on, you close the circuit, vice versa



What kind of car does a electrician drive?

Circuit Properties



Volts-Wagon!!!


Open Circuit

VS.


Closed Circuit

- Open circuits do not allow an electrical current to flow through the circuit.
 - Air is not a good conductor, therefore the electricity cannot flow through to the next component or wire.

Closed circuit

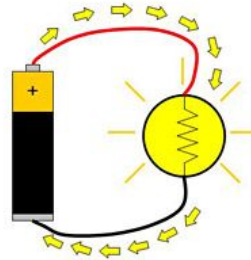

Open circuit

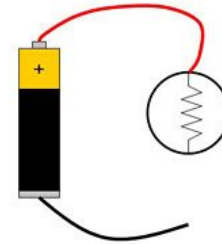


- Closed circuits are complete and allows electricity to flow through.

Series

vs.

Parallel

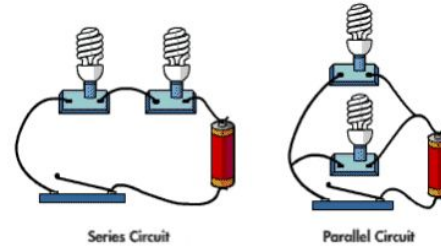- In a series circuit, the electrical components share a current flow and have common nodes.



- In a parallel circuit, the electrical current splits paths and comes back to the negative terminal of the power source.


Kirchhoff's Laws



Gustav Robert Kirchhoff
(1824-1887)


- ❑ German physicist who created laws to calculate currents, voltages, and more
- ❑ also extended the theory of Georg Ohm

Kirchhoff's Current Law (KCL)

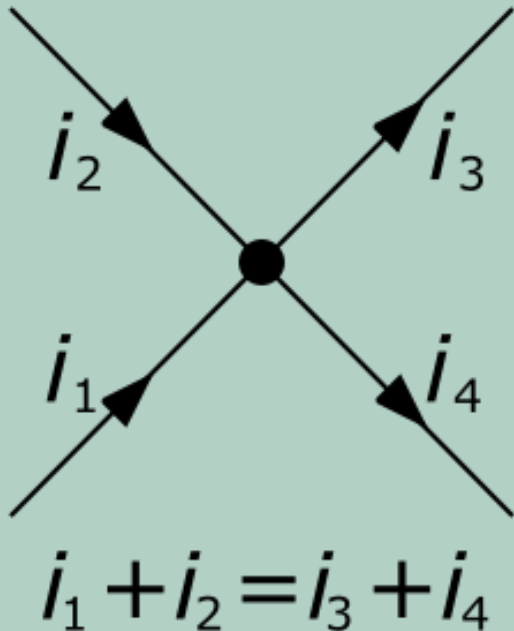

- ❑ the sum of all currents entering a node is equal to the sum of those leaving
- ❑ based on conservation of charge
- ❑ also referred to as the junction rule
- ❑ can be used to solve for I, V, and R in a circuit with unknown quantities

Kirchhoff's Voltage Law (KVL)

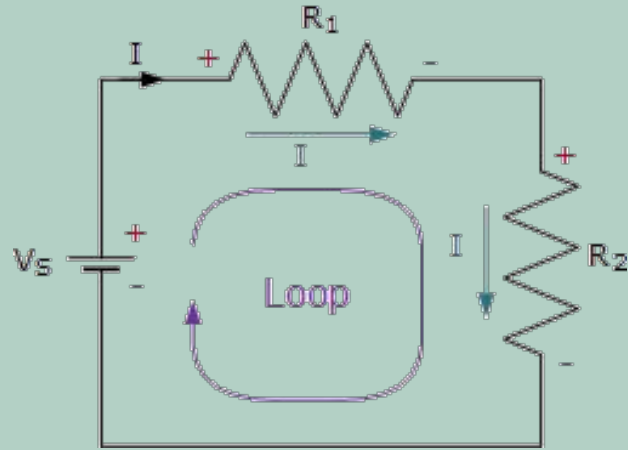

- ❑ the sum of all voltage changes around a complete path is equal to 0
- ❑ based on the conservation of energy
- ❑ similar to displacement
- ❑ can be used to solve for I , V , and R in a circuit with unknown quantities
- ❑ also referred to as the loop rule

What do you call a detective electrician?


More About Circuits



Sherlock Ohms!

What is a Short Circuit?

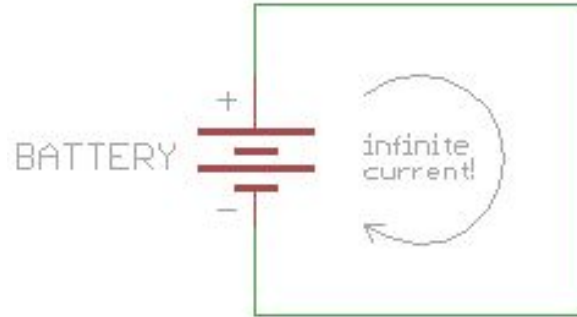A short circuit is when you connect a wire directly from the positive end to the negative end of the power supply. **DO NOT DO THIS!** This can cause explosions.





Circuits and Our Lives

Circuits are incorporated into our lives in many ways. They are used in nearly every type of item that uses electricity, from a phone to a lamp.

What did the baby light bulb say to the
momma light bulb?

I love you watts and watts!



Example of a Circuit




```
1  #include<stdio.h>
2  #include<conio.h>
3  void main()
4  {
5  int num,i,j;
6  printf("Enter a number below 100\n");
7  scanf("%d",&num);
8  for(j=1;j<=2;j++)
9  {
10 for(i=1;i<100;i++)
11 {
12     printf("%d\n",i);
13     if(i==num)
14         break;
15 }
16 }
17 getch();
18 }
19
```



Another Example of a Circuit

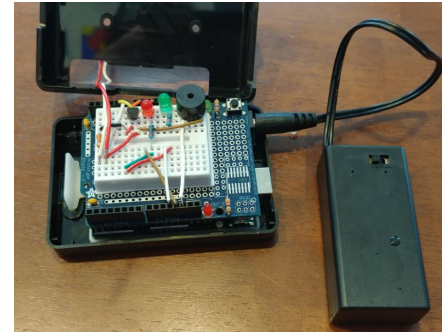Another example of a circuit is a device I built with a few of my classmates at school for a competition. It will alert the guardian of an child if it is too hot inside the car for the child via a buzzer and LED lights. This device uses a pressure sensor, a temperature sensor, and the alert system. It uses a battery as the power source.





Thank You!

Shoutout to Aixa, Catherine, Cynthia, and Dora for being wonderful coordinators and teachers, teaching us about computer science and engineering!