

MODULE 3: Basic Circuits - Resistance

SUMMER CHALLENGE

Electrical Engineering: Smart Lighting

Prachi Shukla

PhD Candidate

Boston University


prachis@bu.edu

Overview

- Circuits Review
- Resistance and Resistors
- Ohms Law
- Breadboards
- Capacitance
- Experiments
 - Resistive Circuit
 - Voltage Divider
 - RC Circuit


Recap - What is a Circuit?

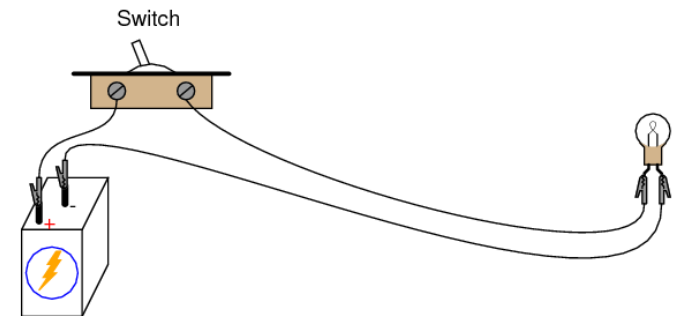- In a circuit, how are the start and end related?
 - They're the same!
- What happens if there isn't a continuous path?
 - Open Circuit – No flow of charge (or electrons)
- What happens when a conduit connects two points?
 - Charge (and electrons) can flow between the points
 - Short Circuit – Directly connecting two points of different voltage
- Switch
 - Device that can open or close a circuit




Resistance

- As charge flows from high to low V , energy is released
 - Where does it go??
- As electrons flow, they encounter *resistance*
 - Generate heat as a result of this opposition
 - Resistance is a function of material, length, and cross-sectional area
 - Resistance is measured in Ohms [Ω]
- Wires have resistance, but it is minimal and a direct connection between different voltage levels is a *short*
- The filament in an incandescent light introduces resistance
 - The heat energy causes the filament to “glow” white-hot and produce light

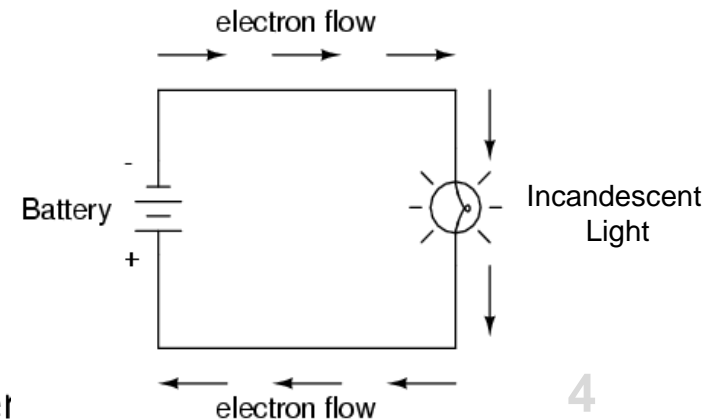

Resistors

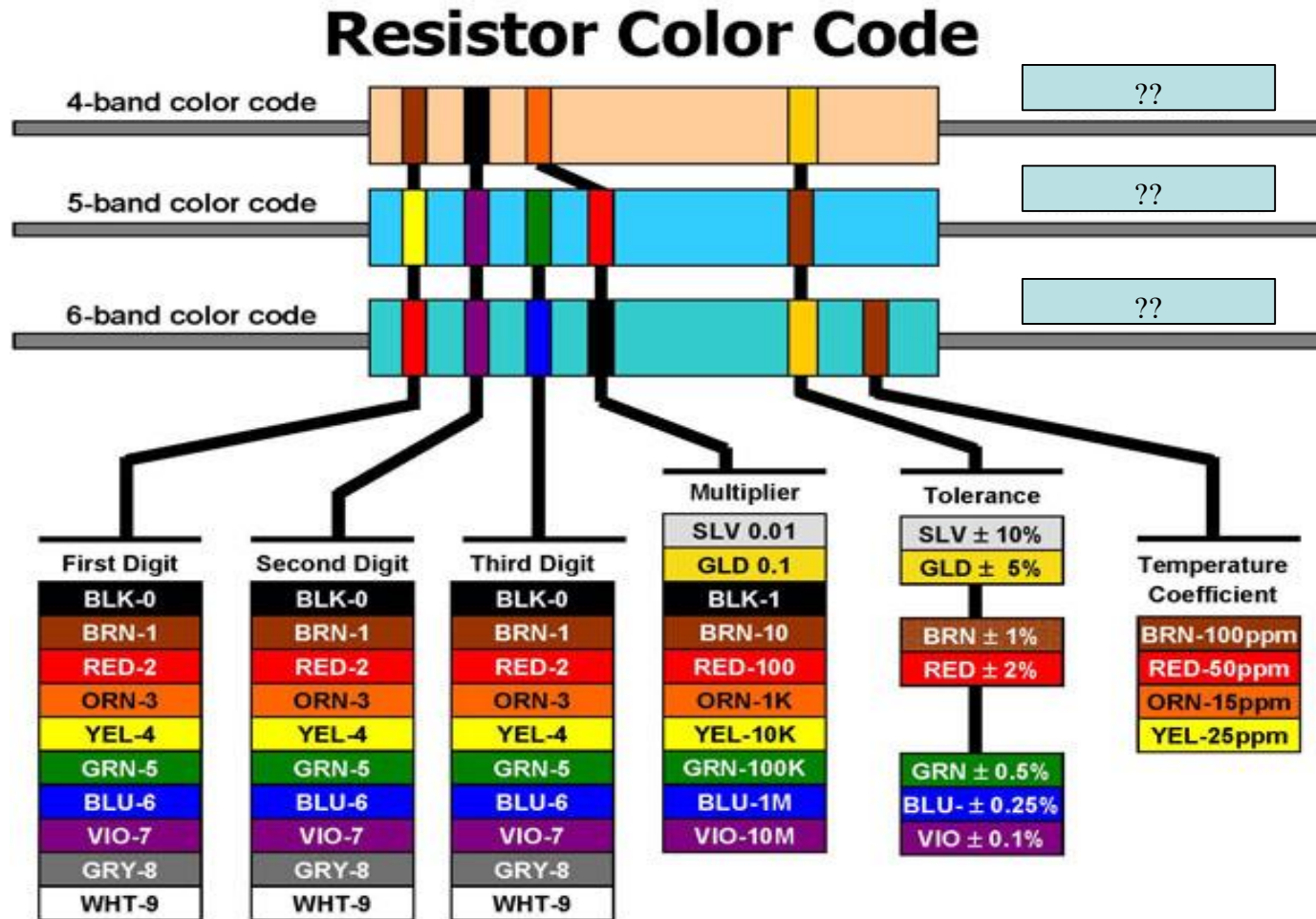

Ohm's Law





$$V = IR$$

- What happens in the case of an open circuit (i.e., $R \approx \infty$)?
- What happens in the case of a short circuit (i.e., $R \approx 0$)?

Series vs Parallel

Series Resistance

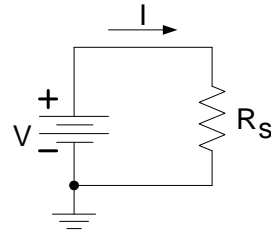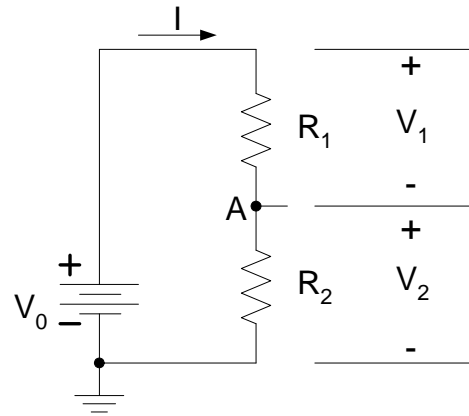



$$V_0 = V_1 + V_2 = IR_1 + IR_2$$

$$= I(R_1 + R_2)$$

$$= IR_s$$

$$R_s = R_1 + R_2$$

Parallel Resistance


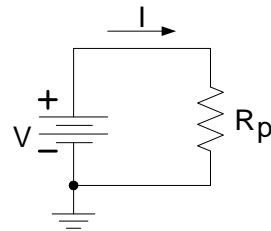
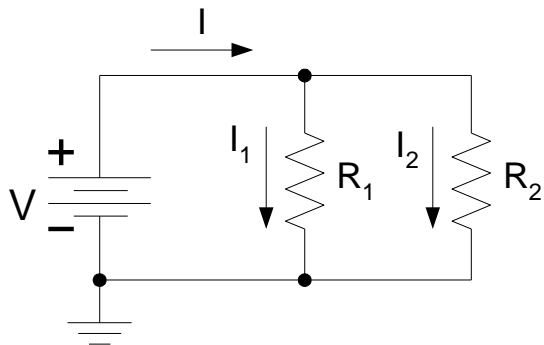


$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_p}$$



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_p = \frac{R_1 R_2}{R_1 + R_2}$$

Breadboards

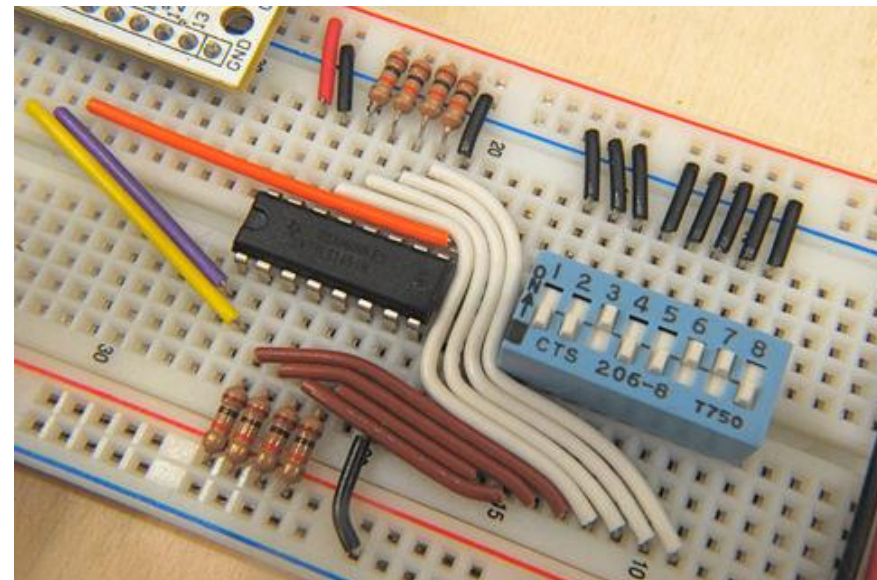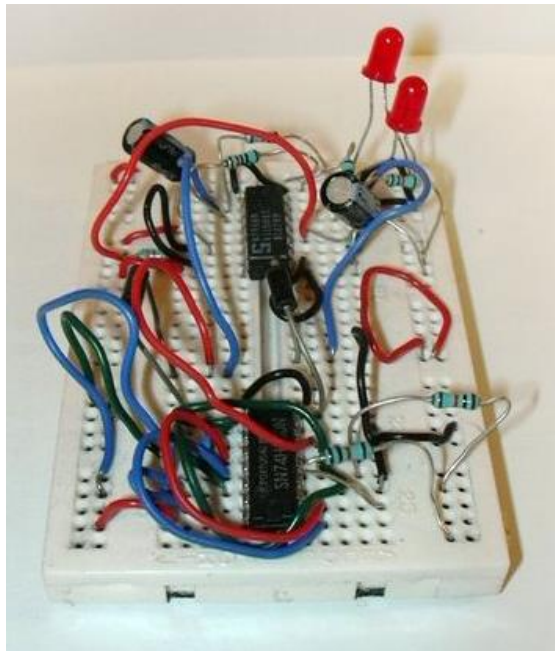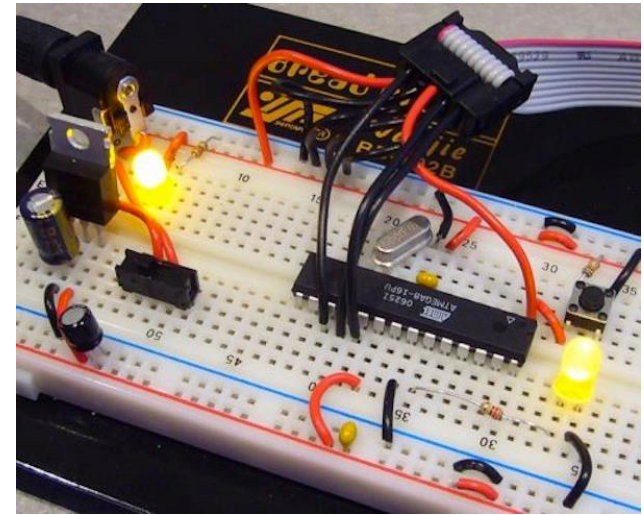- Why do we use breadboards?
 - Temporary Circuits
 - Prototyping
 - No Soldering





Anatomy of a Breadboard

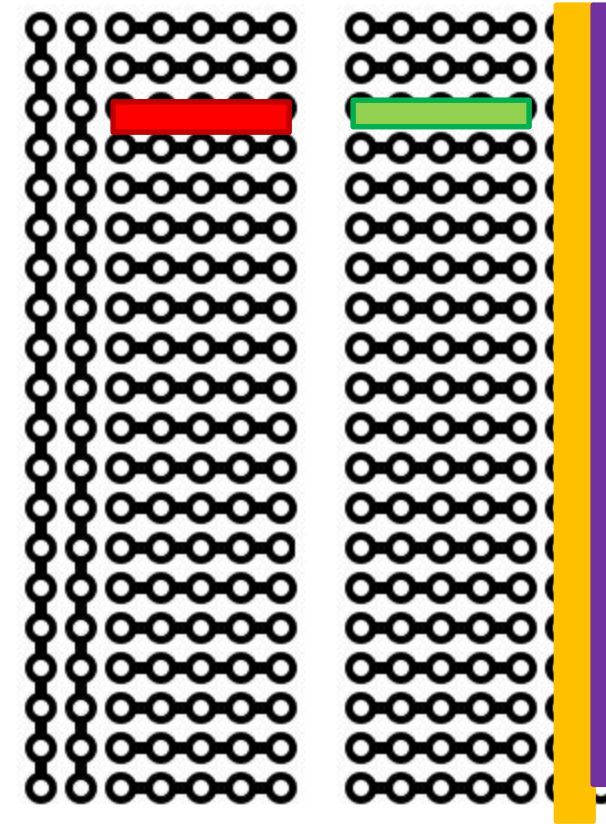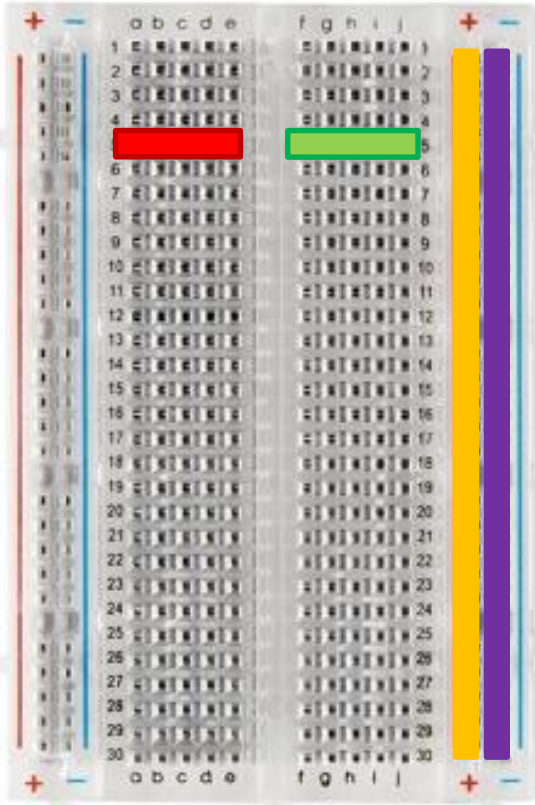


Schematics and Breadboards


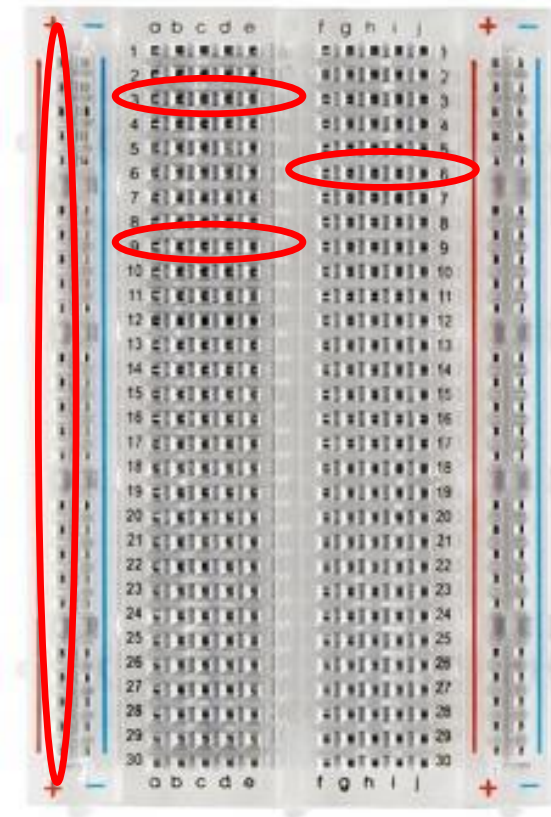
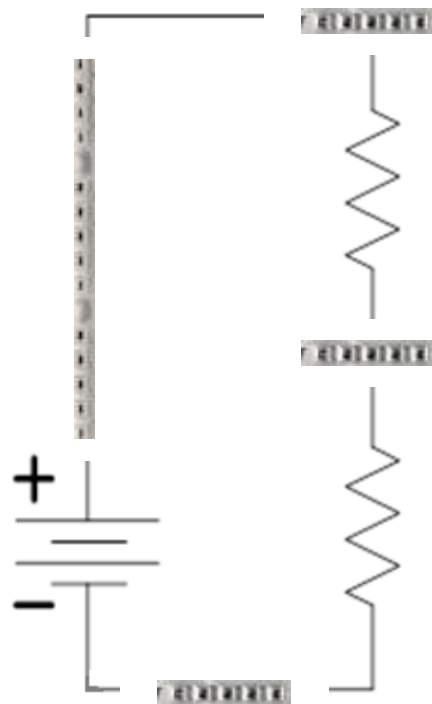
- Connect nodes of a schematic to a connected row of the breadboard




Schematics and Breadboards

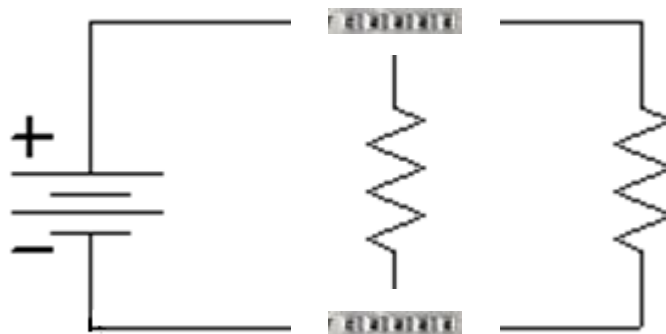- *Connect nodes of a schematic to a connected row of the breadboard*




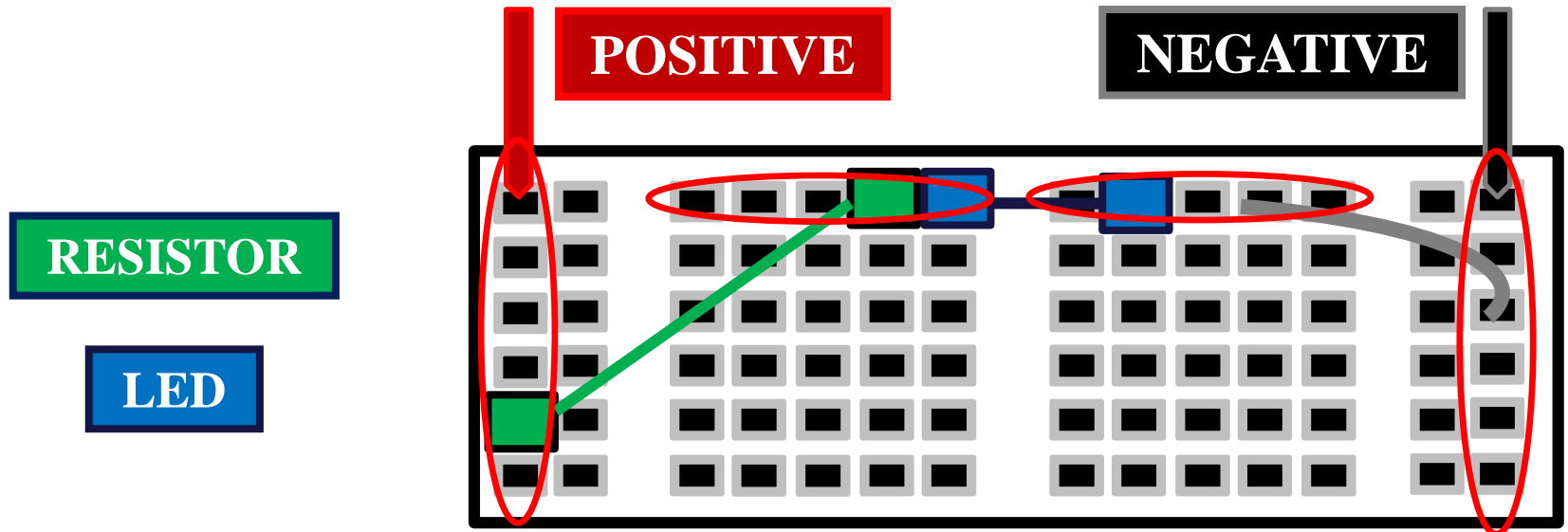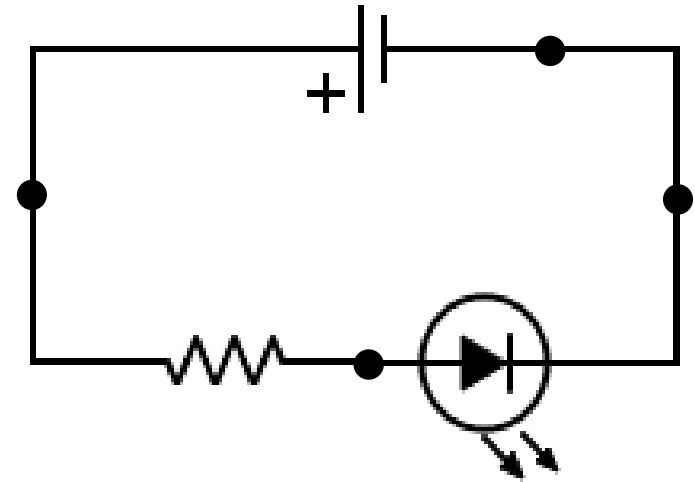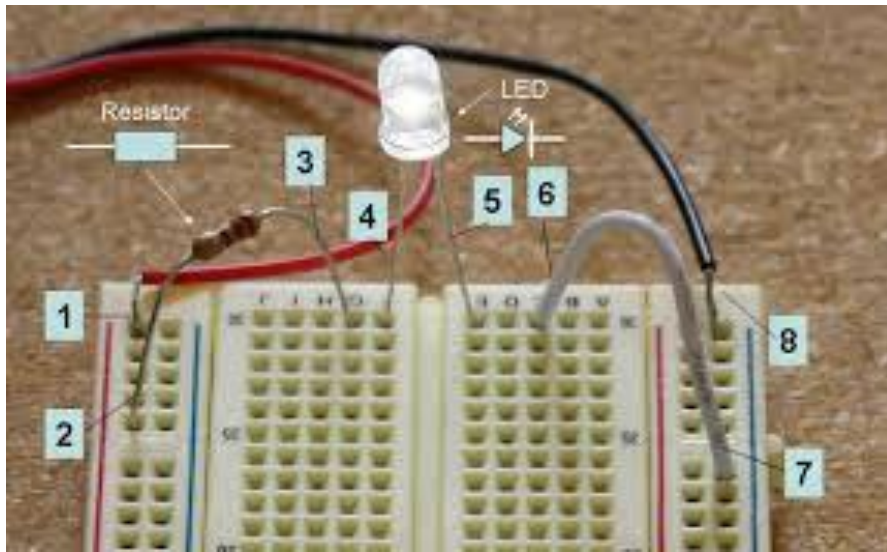

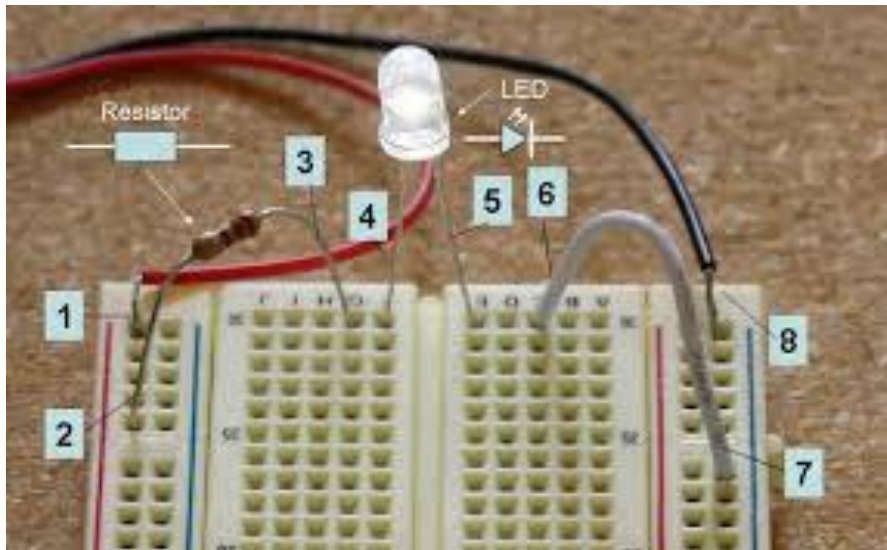


SHORT EXERCISE

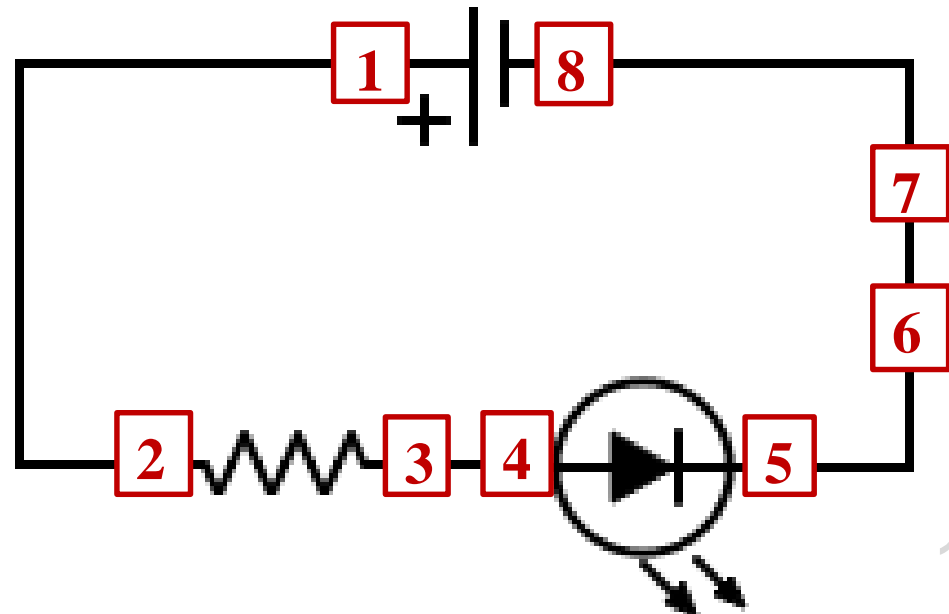1. Copy the schematic.
2. Label where each of the numbers are.



Voltage Divider Circuit

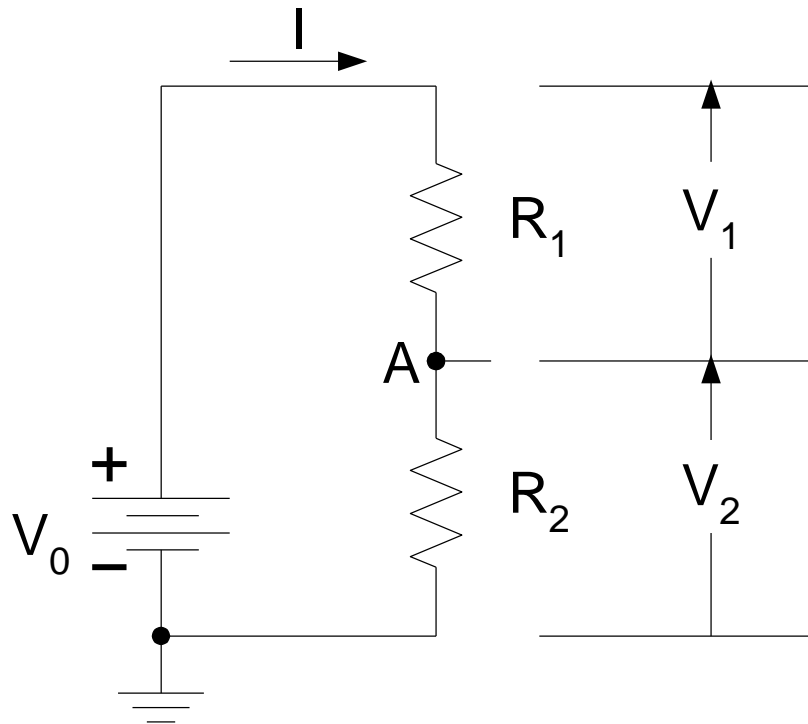

$$I = \frac{V_0}{R_s} = \frac{V_0}{R_1 + R_2}$$

$$V_2 = IR_2 = \frac{V_0}{(R_1 + R_2)} R_2$$

Also
$$V_1 = \frac{R_1}{(R_1 + R_2)} V_0$$

$$V_2 = \frac{R_2}{(R_1 + R_2)} V_0$$

Experiment I

- Voltage Divider
- Resistive Circuits

Recap

- What did you **LEARN** today?

