

MODULE 3: Basic Circuits – Resistance and Capacitance

SUMMER CHALLENGE

Electrical Engineering: Smart Lighting

Prachi Shukla

PhD Candidate

Boston University


prachis@bu.edu

Overview

- Recap
 - Resistance and Resistors
 - Ohms Law
 - Breadboards
- Capacitance
- Experiments
 - Resistive Circuit
 - Voltage Divider
 - RC Circuit


Resistors

Resistor Color Code

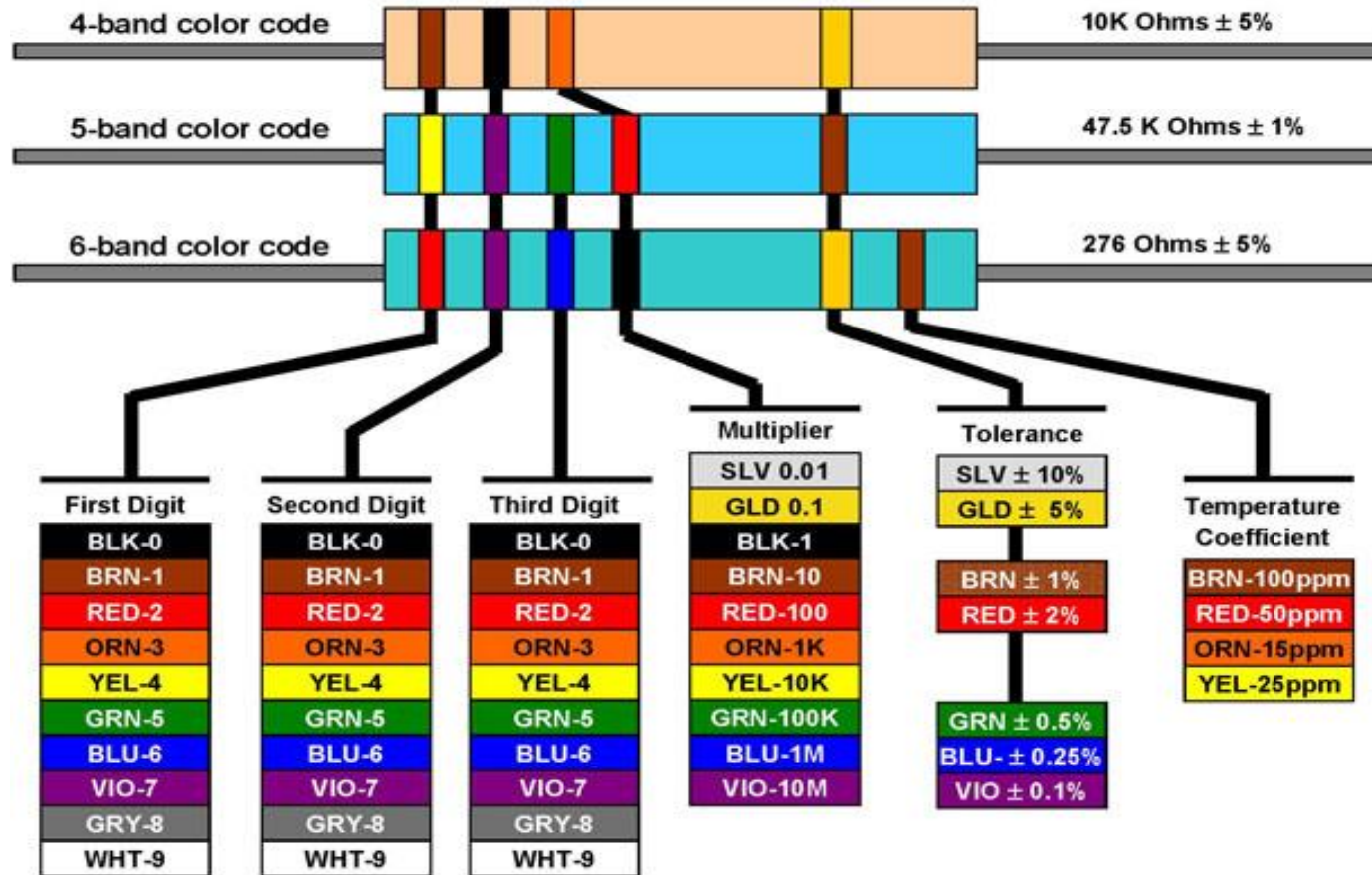

Ohm's Law


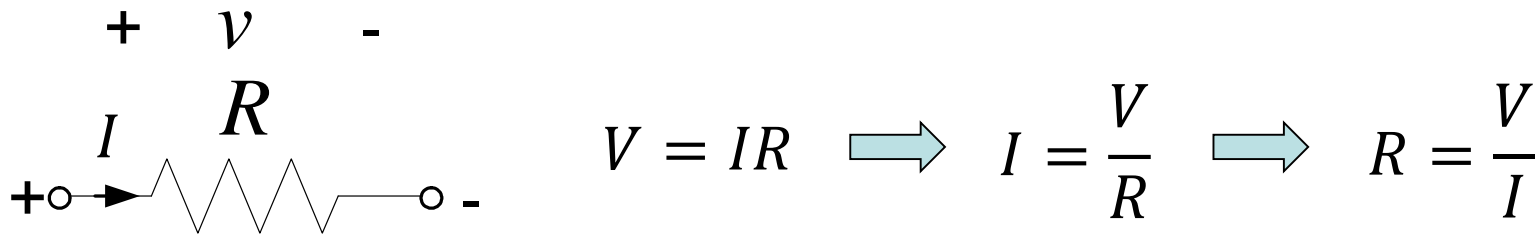
- **Ohm's Law:** Voltage across a resistor is directly proportional to the current flowing through it.
- The proportionality constant is the resistance!



$$V = IR$$

Series vs Parallel

Series Resistance

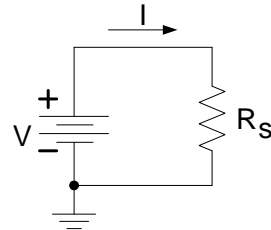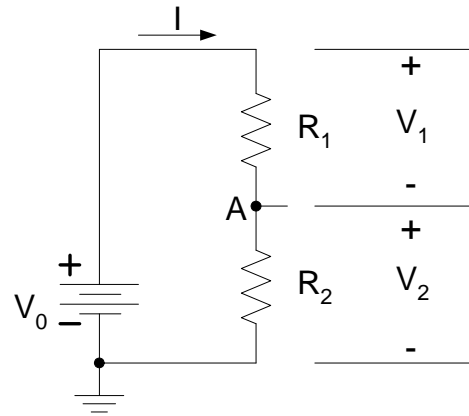



$$V_0 = V_1 + V_2 = IR_1 + IR_2$$

$$= I(R_1 + R_2)$$

$$= IR_s$$

$$R_s = R_1 + R_2$$

Parallel Resistance

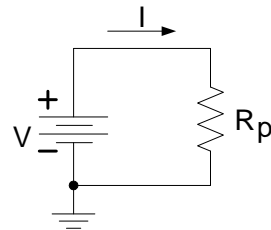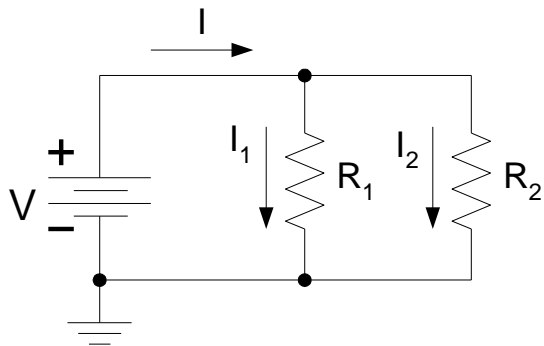



$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_p = \frac{R_1 R_2}{R_1 + R_2}$$


Breadboard

Why do we use breadboards?

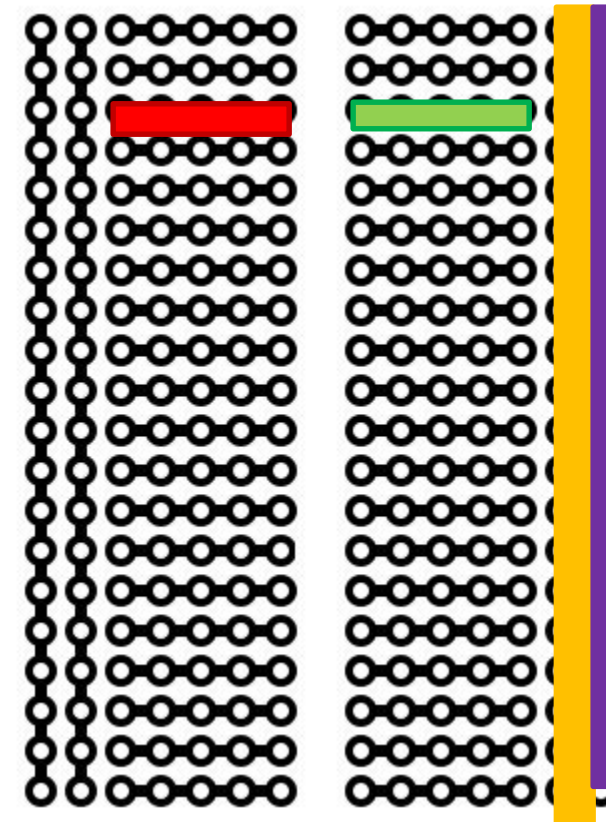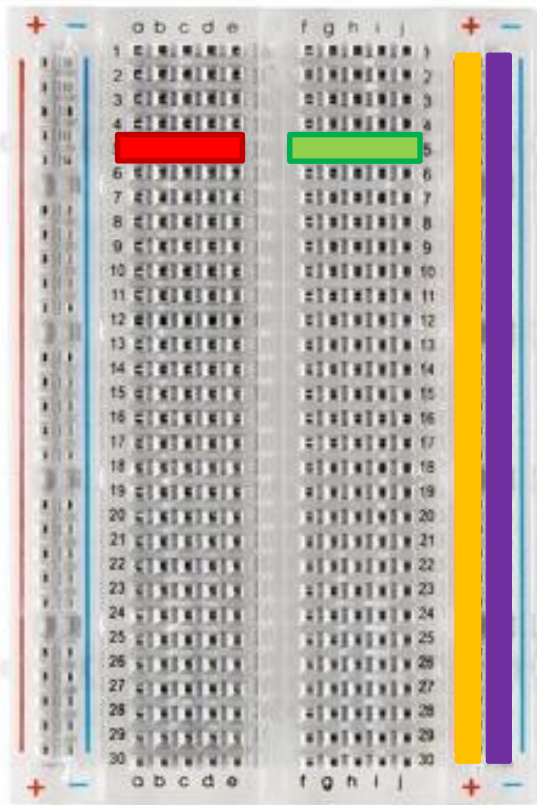Temporary circuits, prototyping, no soldering



Voltage Divider Circuit

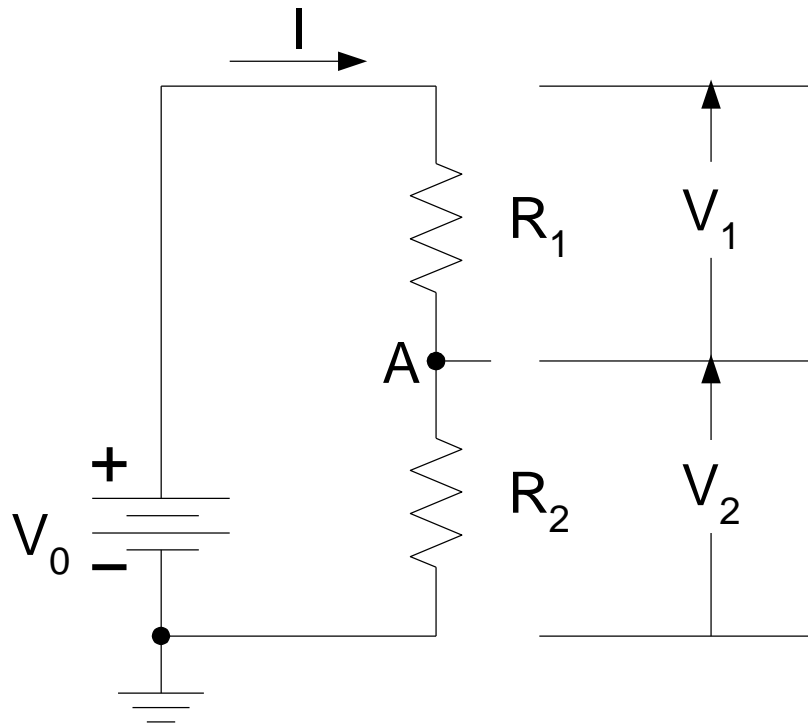

$$I = \frac{V_0}{R_s} = \frac{V_0}{R_1 + R_2}$$

$$V_2 = IR_2 = \frac{V_0}{(R_1 + R_2)} R_2$$

$$\text{Also } V_1 = \frac{R_1}{(R_1 + R_2)} V_0$$


$$V_2 = \frac{R_2}{(R_1 + R_2)} V_0$$

Experiment I

- Voltage Divider
- Resistive Circuits

Capacitors

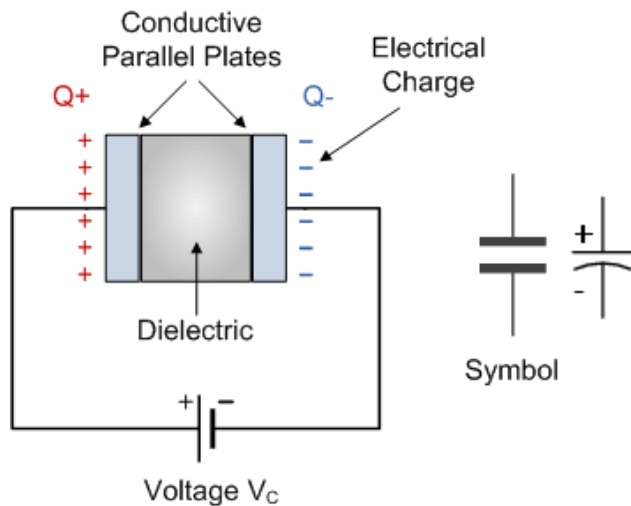- A **capacitor** has capacity to store energy in the form of electrical charge producing a voltage across plates
- Storage of energy is time dependent
 - This was NOT the case in purely resistive circuits.
- Capacitance is measured in Farads [F]



$$i = C \frac{dV}{dt}$$

i = Instantaneous Current
 $\frac{dV}{dt}$ = Instantaneous rate of
 voltage change

Capacitors are *sometimes* polarized

$$C = \frac{\epsilon A}{d}$$

ϵ = dielectric constant
 A = Area of plate overlap
 d = distance between plates

NOTE: Directly connecting a capacitor to a voltage supply isn't practical

Capacitors



- The charge on a capacitor cannot change instantaneously
- The charge on the plates of the capacitor is given as $Q = C \cdot V$
- The current flowing into a capacitor after a long time interval (i.e., steady-state) is zero
 - Charge contained in the capacitor instead of flowing through the circuit

RC Circuits

- RC circuits consist of a resistor and capacitor in series
- A capacitor stores energy and a resistor placed in series with it control the rate at which it charges or discharges.

$$\tau \equiv RC$$

$$V_c = V_s(1 - e^{-t/\tau})$$

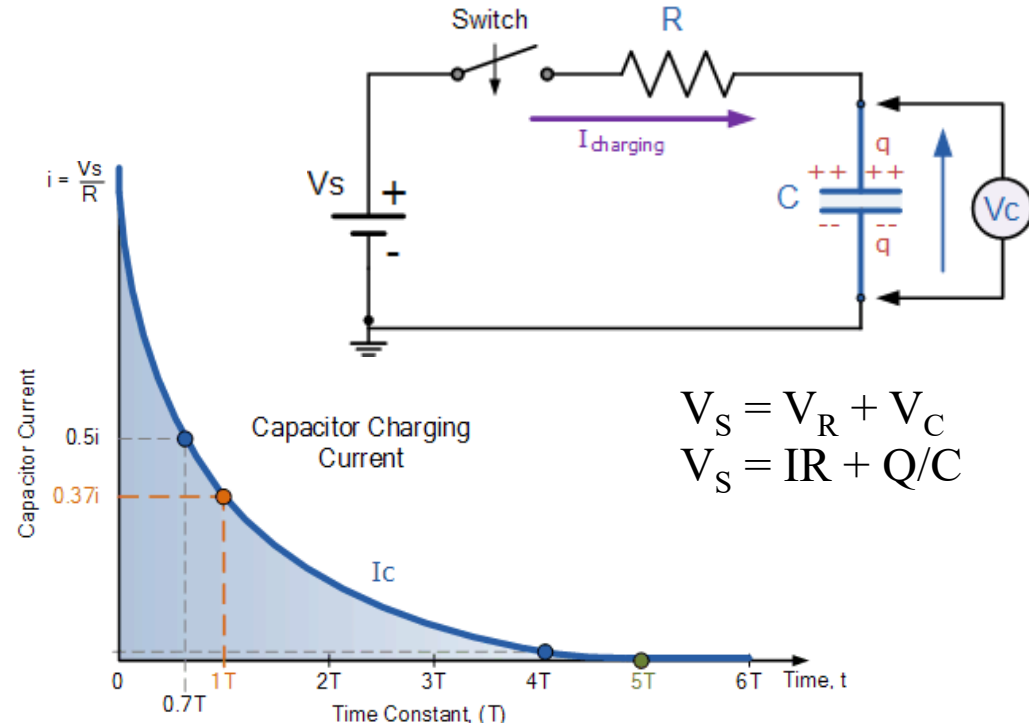
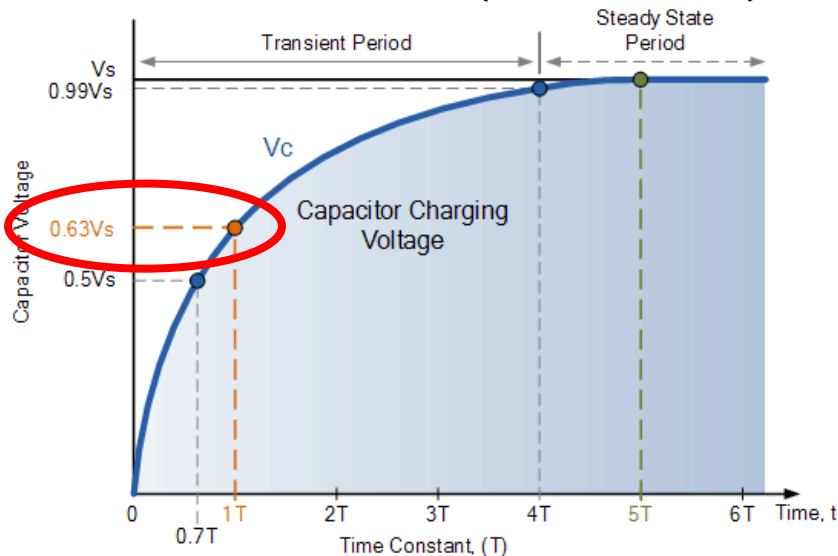


$$V_S = V_R + V_C$$



$$V_S = IR + Q/C$$

RC Circuits

Charge

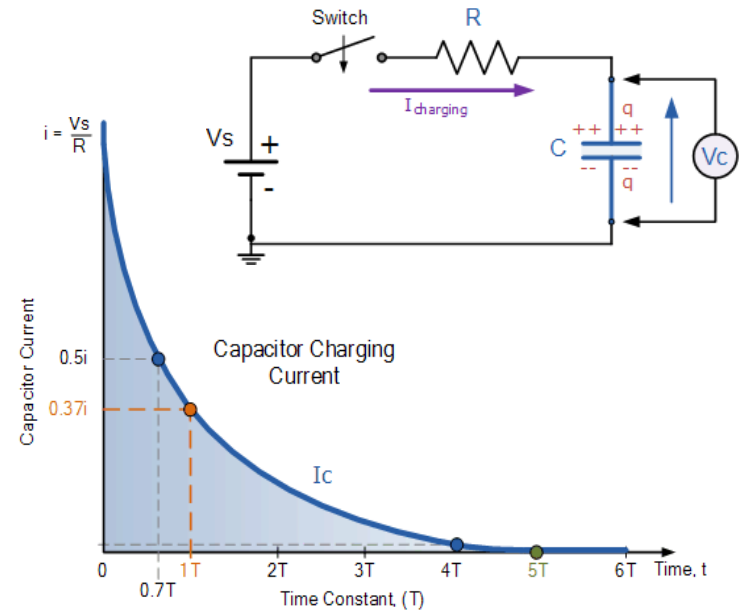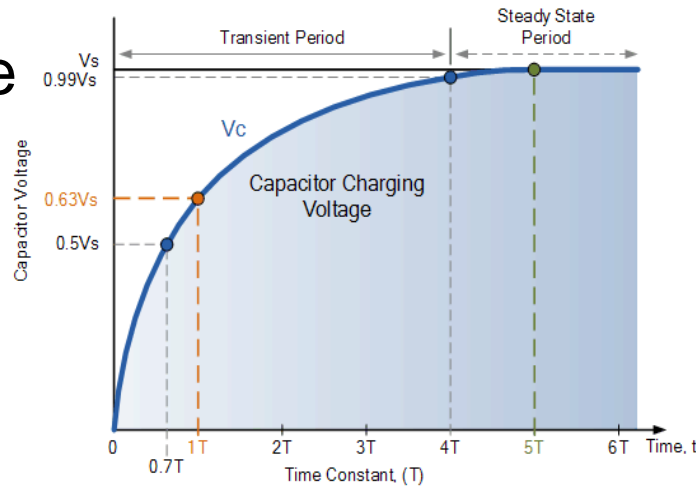

Discharge

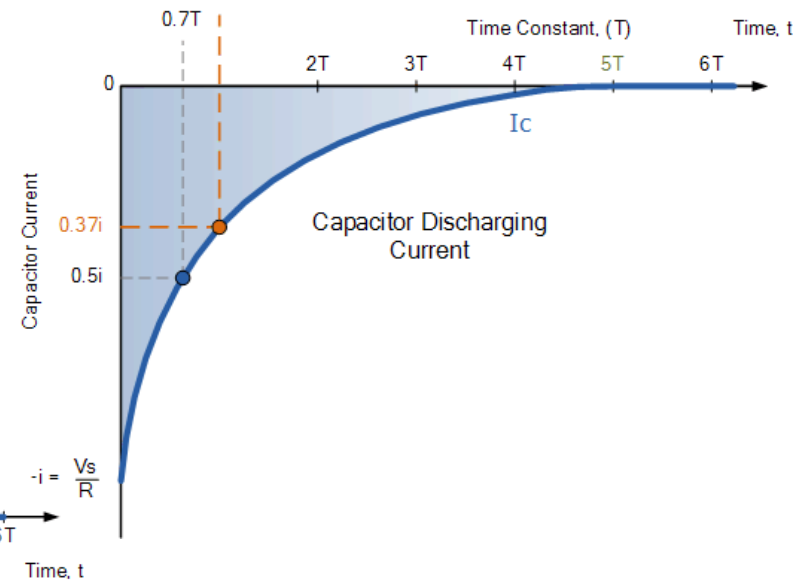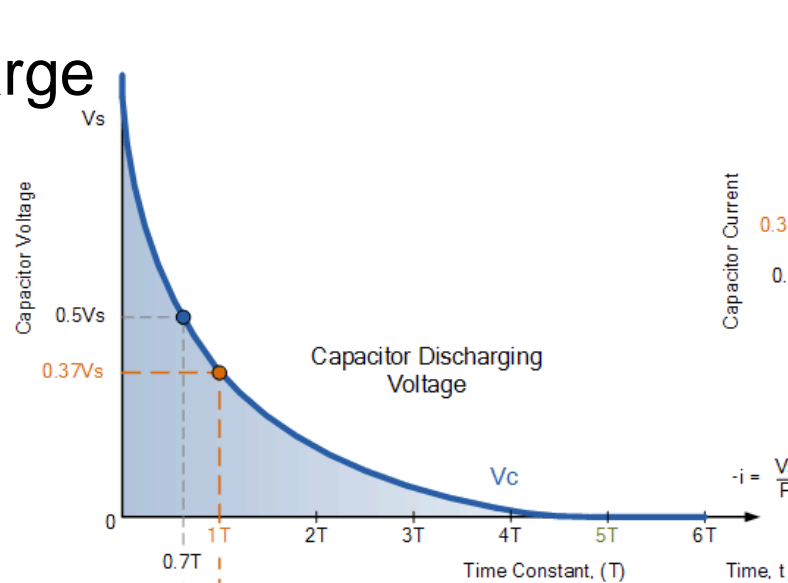

Experiment II

- Resistor – Capacitor (RC) Circuits

Recap

- What did you **LEARN** today?

