

MODULE 4: LEDs

SUMMER CHALLENGE

Electrical Engineering: Smart Lighting

Prachi Shukla

PhD Candidate

Boston University


prachis@bu.edu

Overview

- From “Lighting” to Smart Lighting
- What is a Diode?
- LEDs!
- Electrical Power
- LED Drivers





Lighting & Color Science

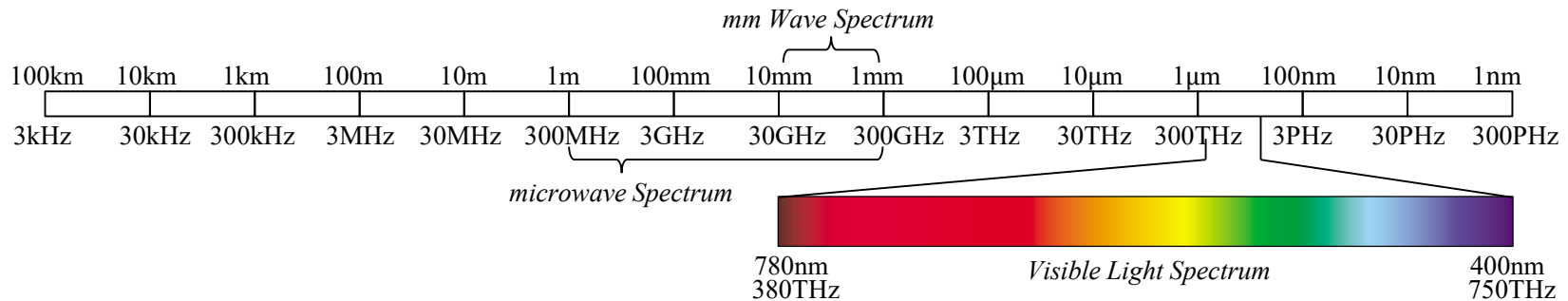- Visible Light is a form of electromagnetic radiation



- The human eye responds to the visible light spectrum
- White light is the presence of all colors


Human-Eye Response

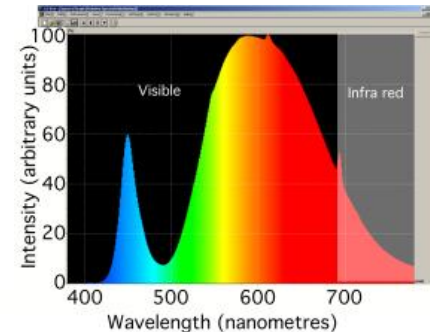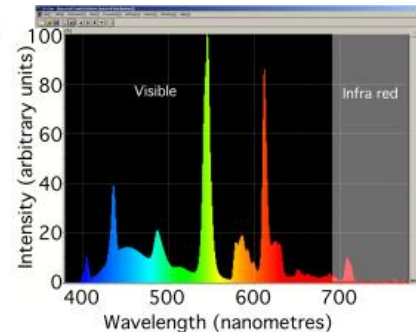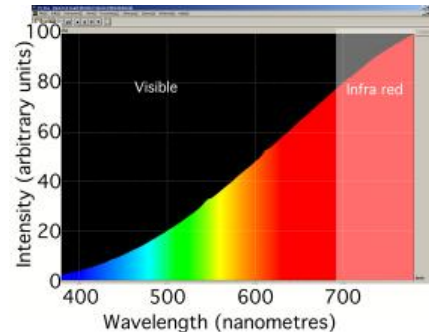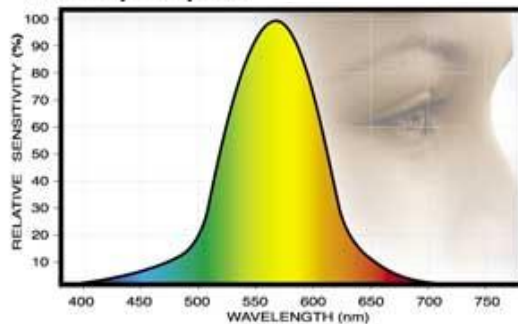




Smart Lighting

■ In what ways can light be better?


■ Energy Efficiency

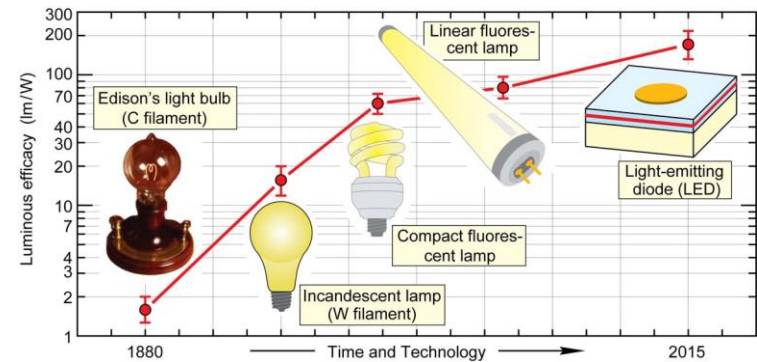

■ Healthy Lighting

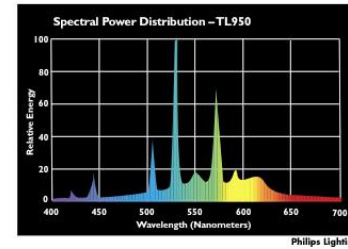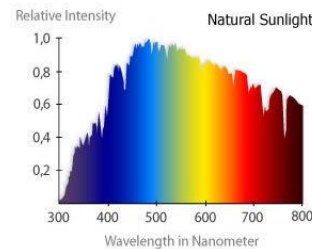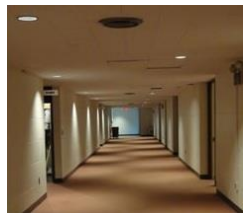

■ Productivity (Data access)

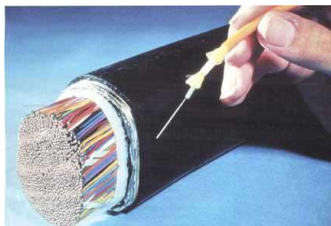



What is a diode?

- A device that allows current to flow in *one* direction; always has polarity (e.g., LED)



Forward Bias Voltage

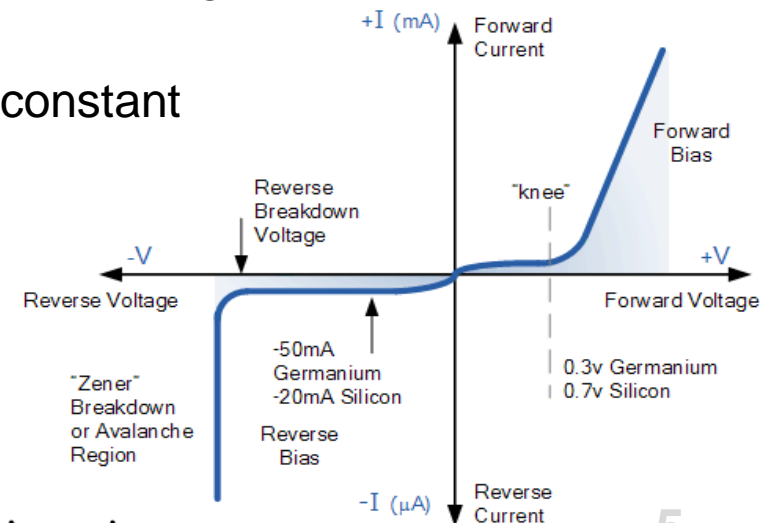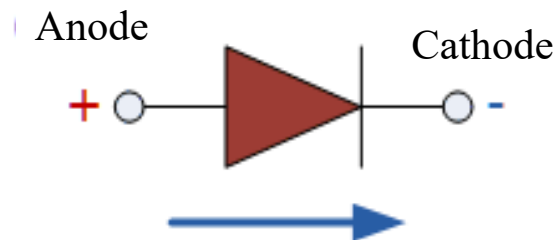
- For current to flow, diodes require a turn-on voltage (i.e., forward bias voltage)
- In an *ideal* diode, voltage drop remains constant



Kirchhoff's Voltage Law

- The algebraic sum of all voltages in a loop must equal 0


$$V_0 + (-V_1) + (-V_2) = 0$$

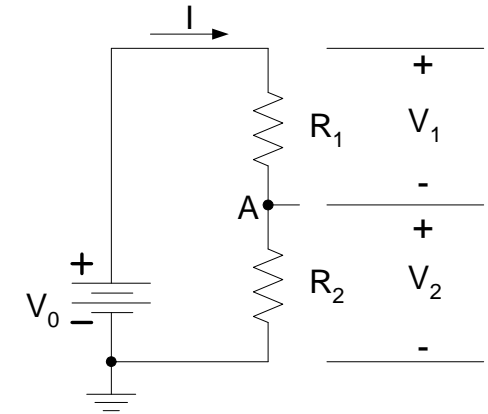

- Relationship to Diode circuits

- Once the diode reaches the turn on voltage, V_R increases with V_S
- Current through the circuit increases with increase in $V_R + V_D$

$$V_S + (-V_D) + (-V_R) = 0$$

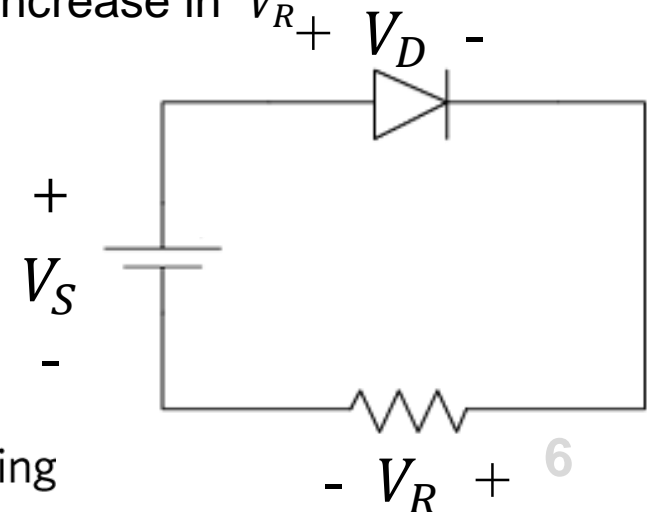

LEDs



David Miller

How Do LEDs Work?

■ LED Materials

- Semiconducting materials: Resistance levels between those of a conductor and an insulator
- Current can only flow in one direction

■ Passing through the LED, electrons lose energy

- Lost energy creates photons
- Photons have discrete wavelength related to band-gap

■ Band-gap width and energy

- The wider the band-gap, the greater the energy of the photon released
- Specialized materials & processes required to achieve wide band-gap
- Planck's Relation:

$$E = \frac{hc}{\lambda}$$



E: Energy

h: planck constant


c: speed of light

λ : wavelength

Small Band Gap: Low Energy Red Light

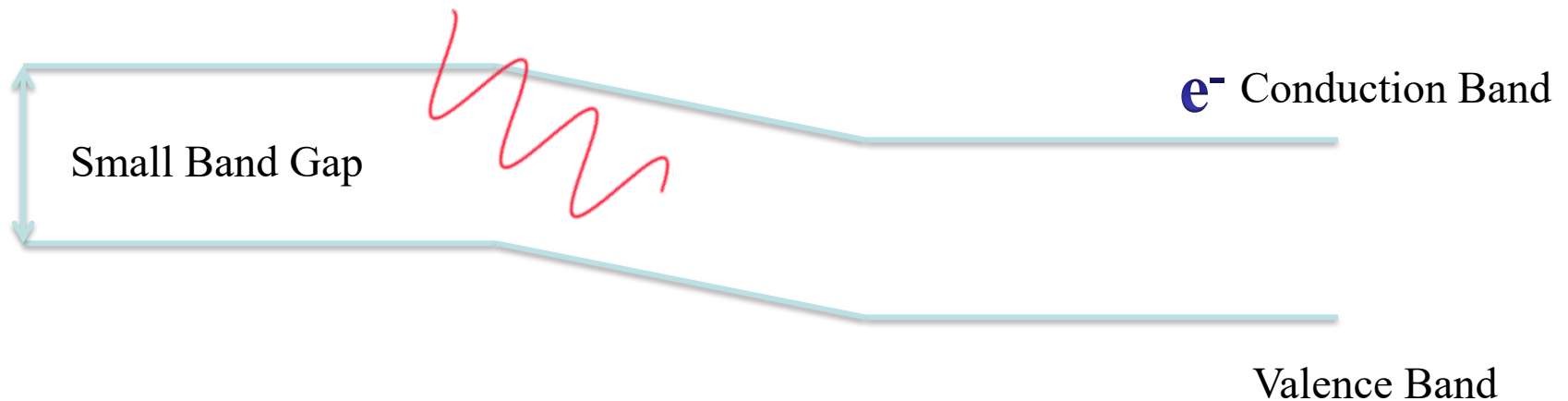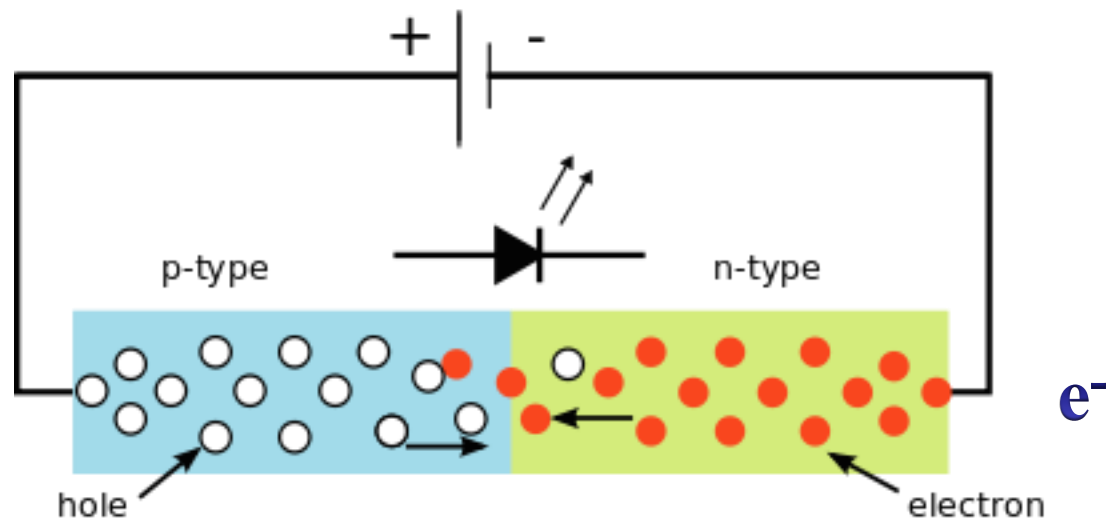

Large Band Gap: High Energy Blue Light

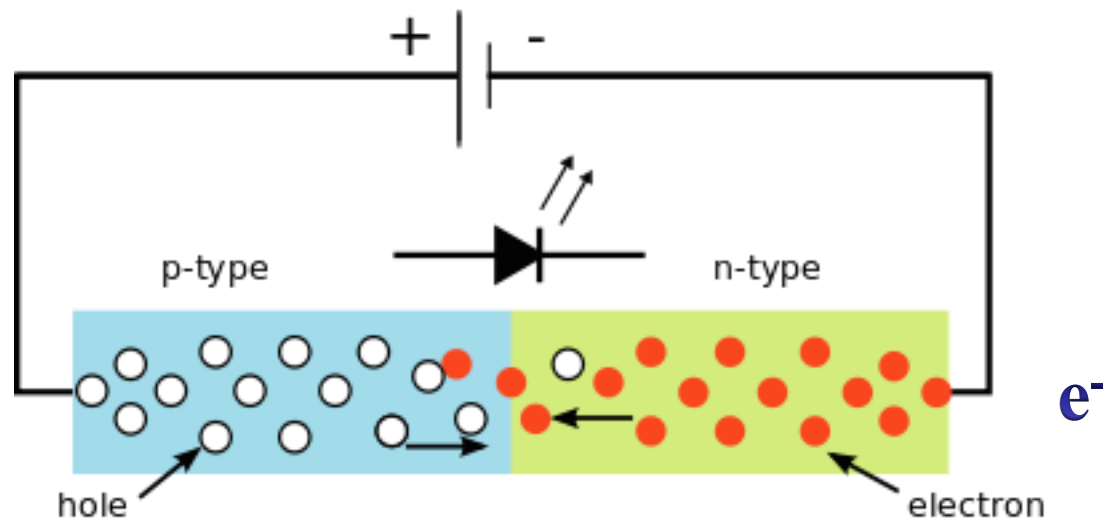

Experiment I

- LED circuit
- Determining the turn-on voltage


Electrical Power

- Power is the rate at which energy is consumed.

$$P = VI$$

← This is another one of those important equations...

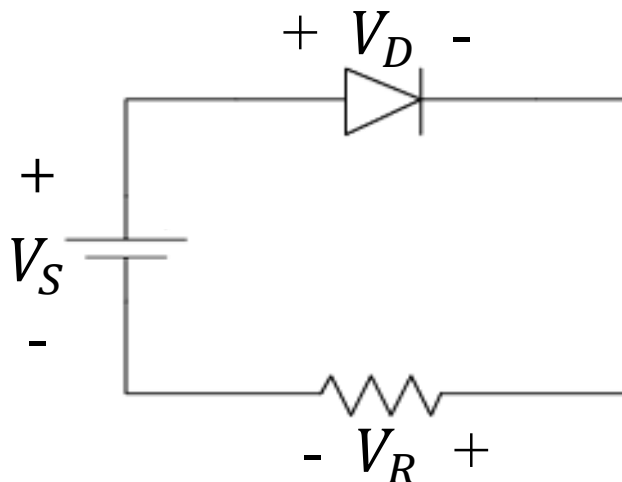- Power is measured in Watts [W] or [J/s]
- Energy *sources* (such as batteries) produce power while the *load* of the circuit absorbs power.



$$I = \frac{V_R}{R} = \frac{V_S - V_D}{R}$$

$$P_D = V_D I = \frac{V_D (V_S - V_D)}{R}$$


Electrical Power

$$V = IR$$

- Combining the previous equation with Ohm's

- Law:
$$P = VI = I^2R = V^2/R$$

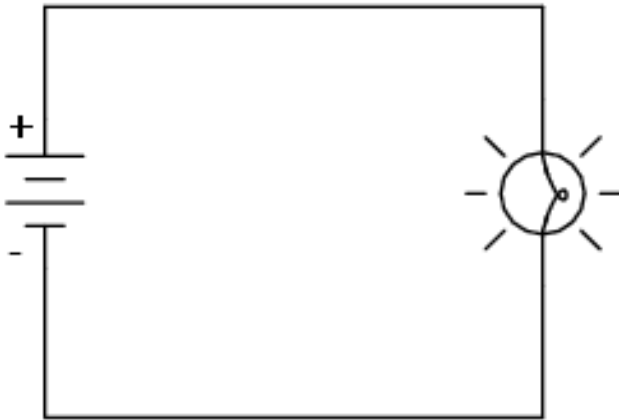- Consider a 60W incandescent attached to a 120V source
 - How does current change if you replace the 60W bulb with 120W bulb?



$$60 = 120I_1$$

$$120 = 120I_2$$

Experiment II

- LED Drivers
- Power Consumption

Recap

- What did you **LEARN** today?

