

MODULE 3: Basic Circuits

BU SUMMER CHALLENGE

Electrical Engineering: Smart Lighting Project



Beste Oztop
PhD Student
Boston University
boztop@bu.edu

Overview

- Circuits Review
- Resistance and Resistors
- Ohm's Law
- Breadboards
- Capacitance
- Experiments
 - Resistive Circuit
 - Voltage Divider
 - RC Circuit


Recap - What is a Circuit?

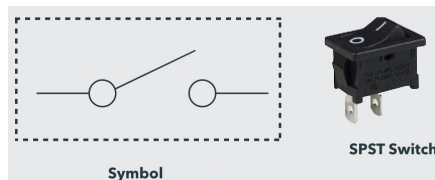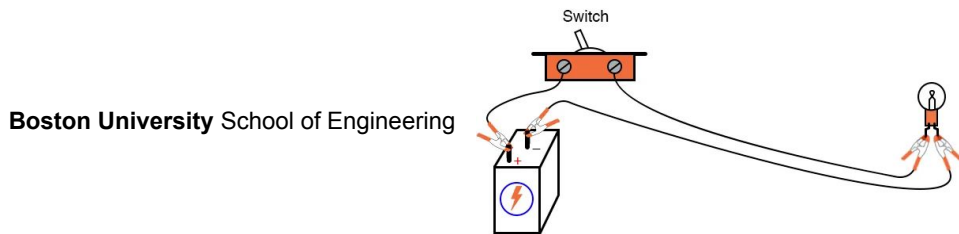- In a circuit, how are the start and end related?
 - They're the same!
- What happens if there isn't a continuous path?
 - Open Circuit – No flow of charge (or electrons)
- What happens when a conduit connects two points?
 - Charge (and electrons) can flow between the points
 - Short Circuit – Directly connecting two points of different voltage
- Switch
 - Device that can open or close a circuit




Resistance

- As charge flows from high to low V , energy is released
 - Where does it go??
- As electrons flow, they encounter resistance
 - Generate heat as a result of this opposition
 - Resistance is a function of material, length, and cross-sectional area
 - Resistance is measured in Ohms [Ω]
- Wires have resistance, but it is minimal and a direct connection between different voltage levels is a short
 - The filament in an incandescent light introduces resistance
 - The heat energy causes the filament to “glow” white-hot and produce light

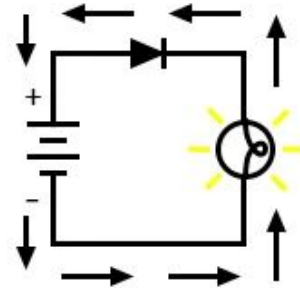

Resistors

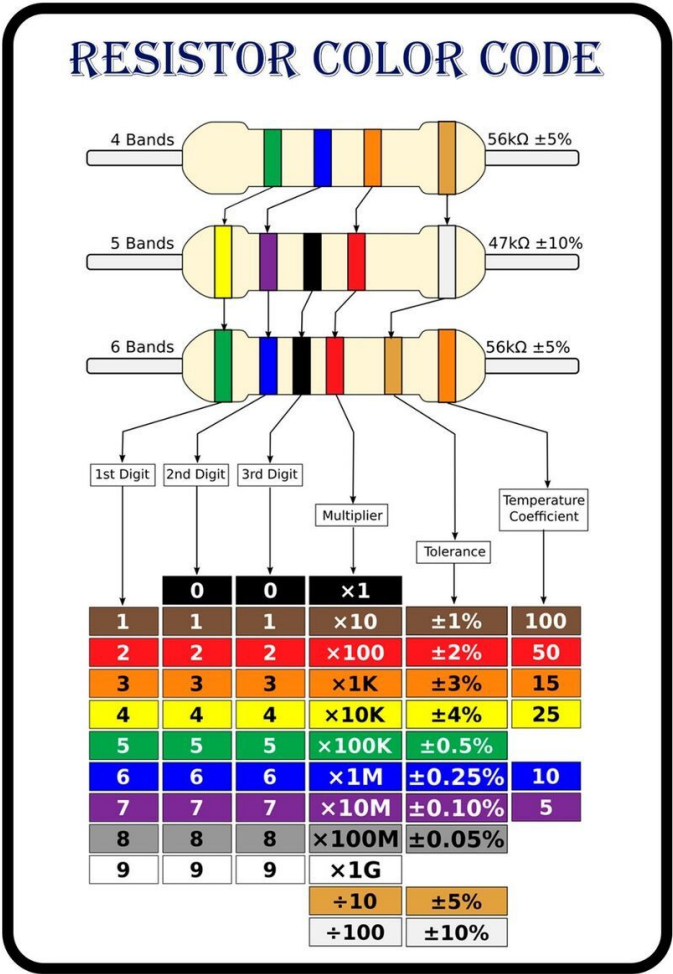

Ohm's Law


$$V = IR$$

What happens in the case of an open circuit (i.e., $R \approx \infty$)?

What happens in the case of a short circuit (i.e., $R \approx 0$)?

Series vs Parallel


Series Resistance

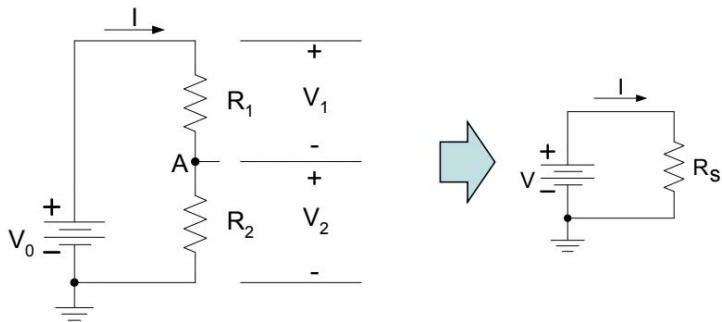

$$\begin{aligned} V_0 &= V_1 + V_2 = IR_1 + IR_2 \\ &= I(R_1 + R_2) \\ &= IR_s \end{aligned}$$

$$R_s = R_1 + R_2$$

Parallel Resistance

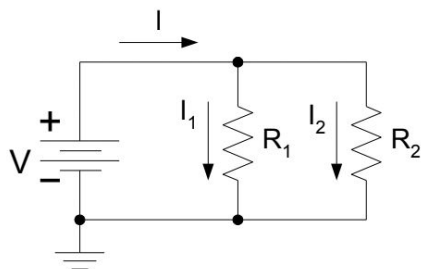




$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

Breadboards

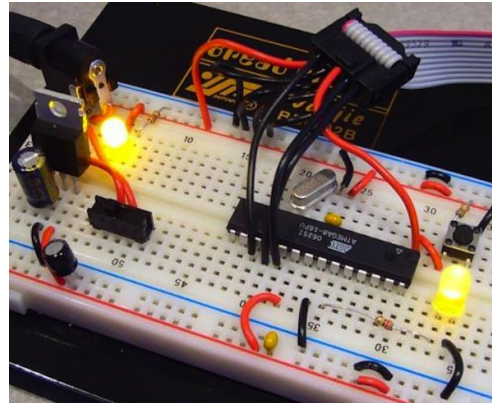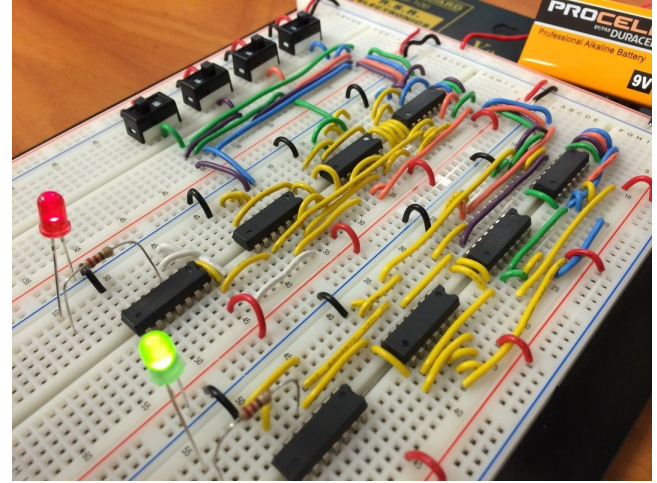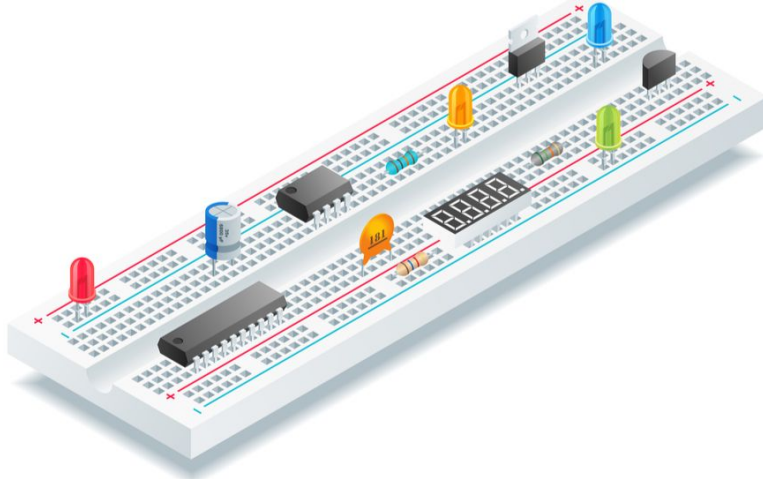- Why do we use breadboards?
 - Temporary Circuits
 - Prototyping
 - No Soldering





Anatomy of a Breadboard

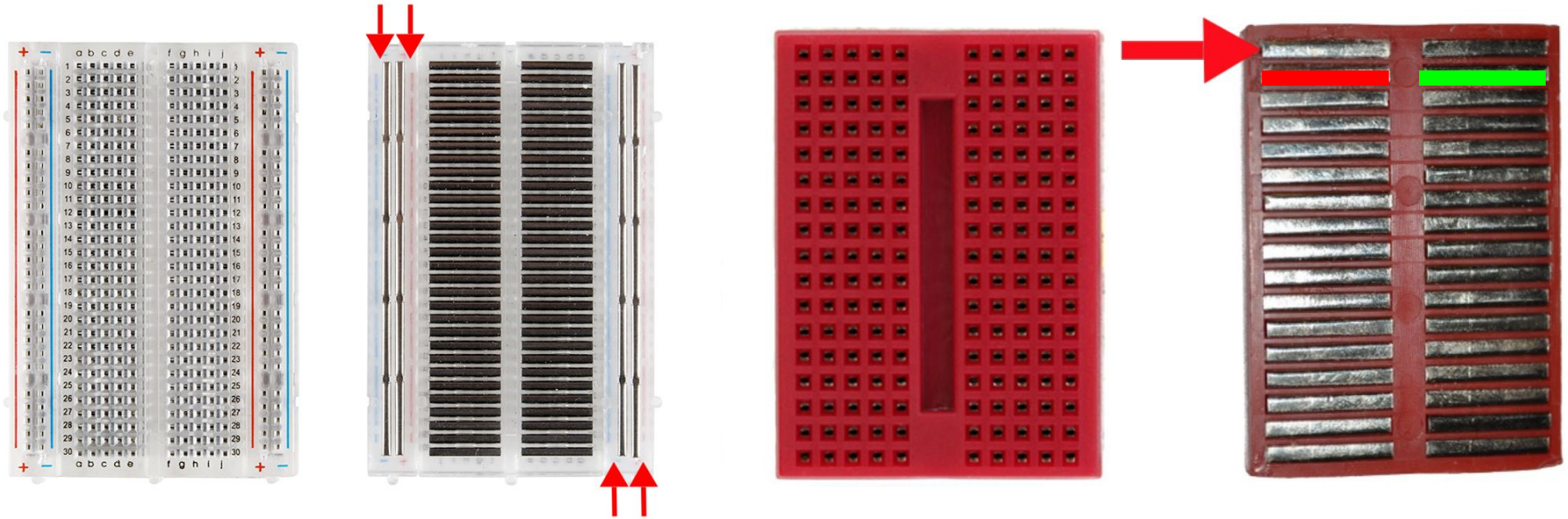


Schematics and Breadboards


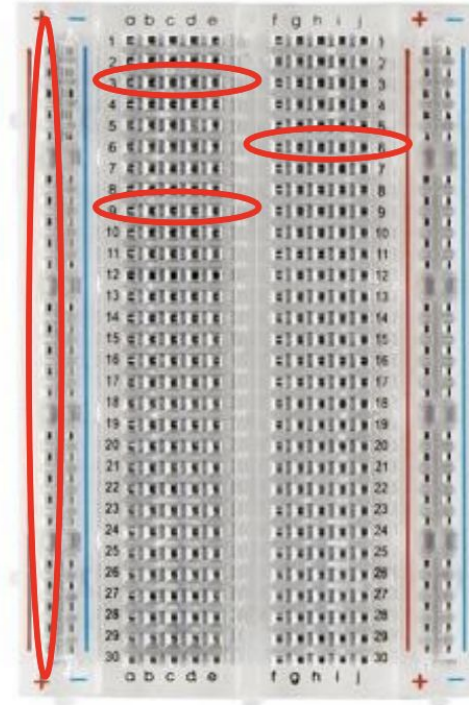
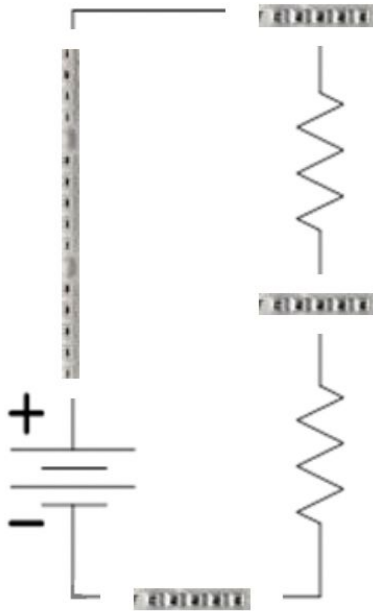
Connect nodes of a schematic to a connected row of the breadboard




Schematics and Breadboards

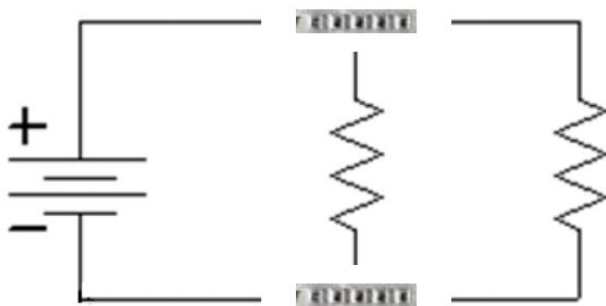Connect nodes of a schematic to a connected row of the breadboard




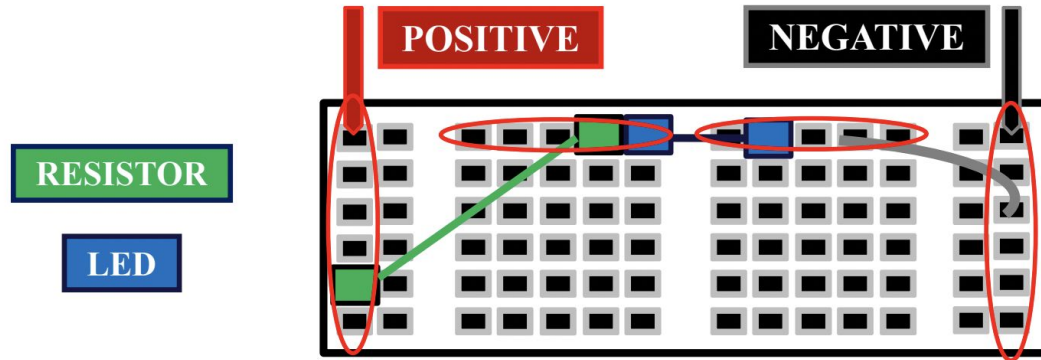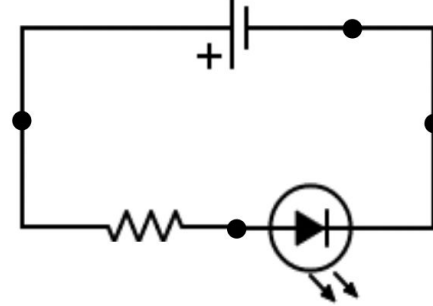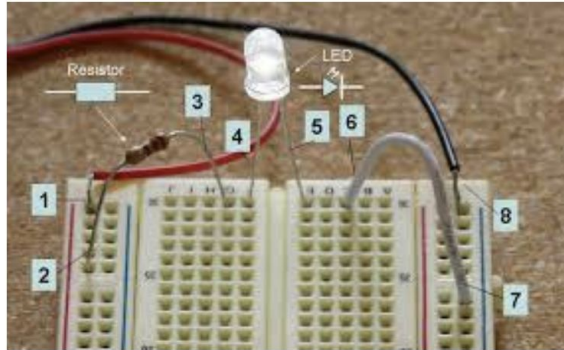

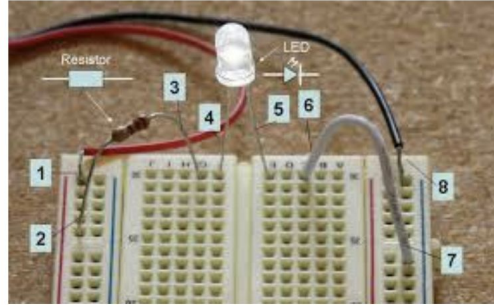


SHORT EXERCISE

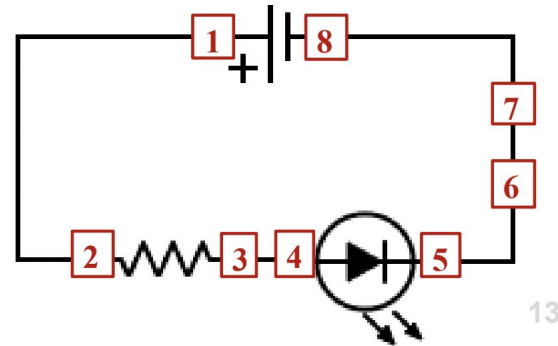1. Copy the schematic.
2. Label where each of the numbers are.



Voltage Divider Circuit

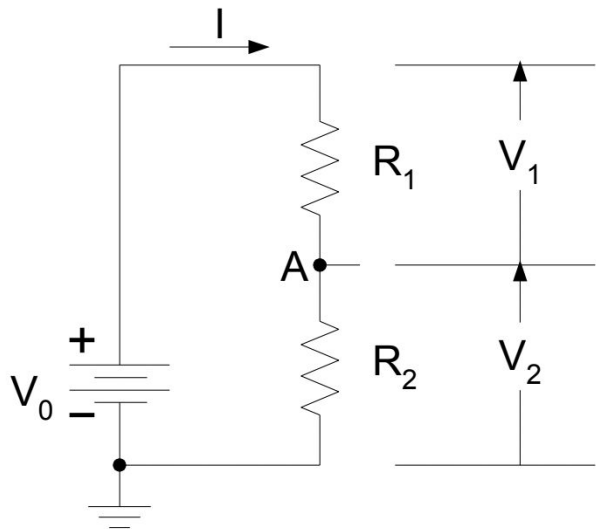

$$I = \frac{V_0}{R_s} = \frac{V_0}{R_1 + R_2}$$

$$V_2 = IR_2 = \frac{V_0}{(R_1 + R_2)} R_2$$

$$\text{Also } V_1 = \frac{R_1}{(R_1 + R_2)} V_0$$

$$V_2 = \frac{R_2}{(R_1 + R_2)} V_0$$

Experiment I

- Go to “**Lab Module 3: Basic Circuits**” in your experiment manual
- Voltage Divider
- Resistive Circuits

★ Reflect on what you learned so far!

- References:

- <http://www.physicsclassroom.com/>
- <http://www.allaboutcircuits.com/>




Overview

- Recap
 - Resistance and Resistors
 - Ohm's Law
 - Breadboards
- Capacitance
- Experiments
 - Resistive Circuit
 - Voltage Divider
 - RC Circuit


Resistors

RESISTOR COLOR CODE

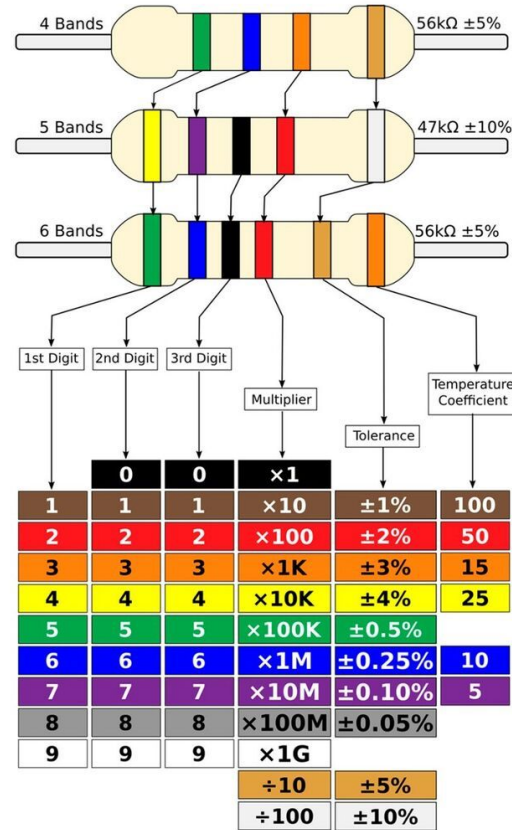

Ohm's Law

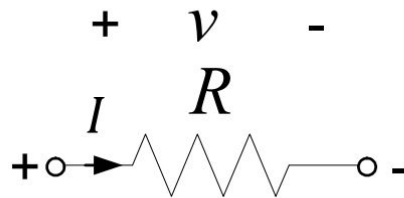- Ohm's Law: Voltage across a resistor is directly proportional to the current flowing through it.
- The proportionality constant is the resistance!




A circuit diagram showing a resistor labeled R . The voltage across the resistor is labeled V with a '+' sign on the left and a '-' sign on the right. The current flowing through the resistor is labeled I with an arrow pointing to the right.

$$V = IR \quad \Rightarrow \quad I = \frac{V}{R} \quad \Rightarrow \quad R = \frac{V}{I}$$

$$V = IR$$

Series vs Parallel


Series Resistance

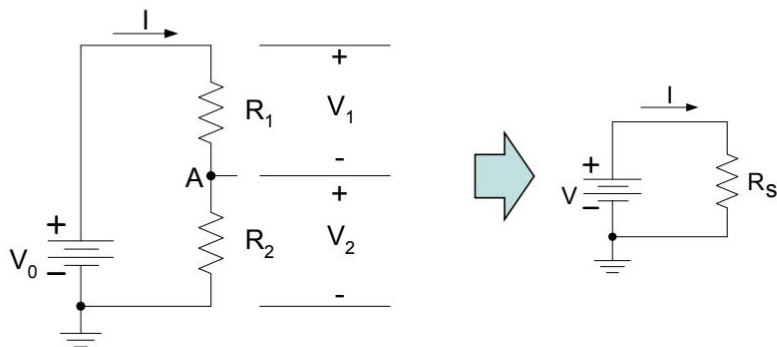

$$\begin{aligned} V_0 &= V_1 + V_2 = IR_1 + IR_2 \\ &= I(R_1 + R_2) \\ &= IR_s \end{aligned}$$

$$R_s = R_1 + R_2$$

Parallel Resistance

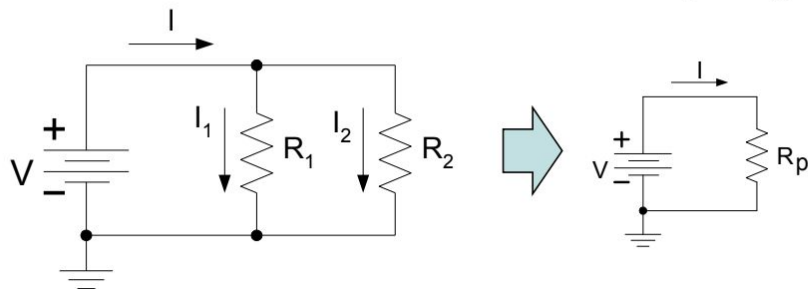




$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

Breadboards

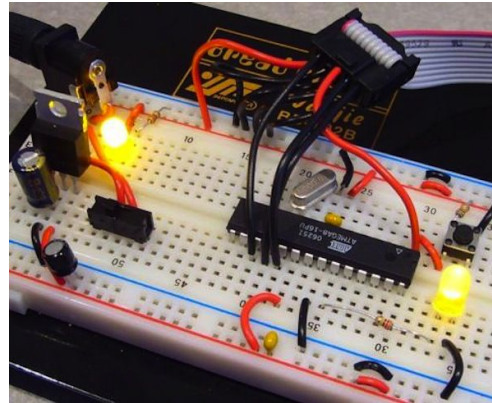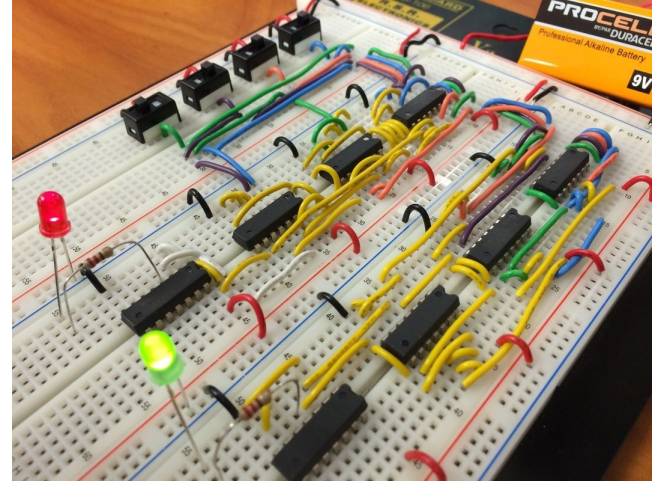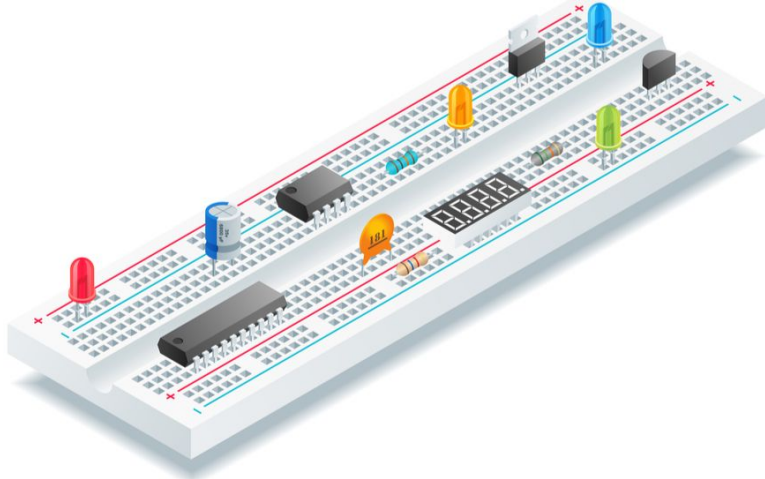- Why do we use breadboards?
 - Temporary Circuits
 - Prototyping
 - No Soldering



Voltage Divider Circuit

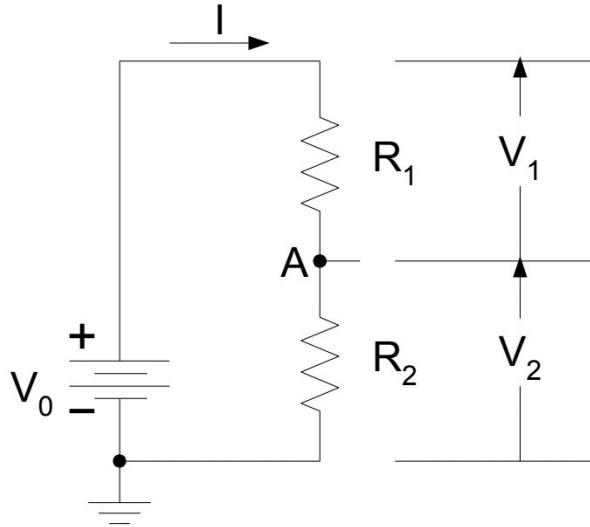

$$I = \frac{V_0}{R_s} = \frac{V_0}{R_1 + R_2}$$

$$V_2 = IR_2 = \frac{V_0}{(R_1 + R_2)} R_2$$

$$\text{Also } V_1 = \frac{R_1}{(R_1 + R_2)} V_0$$

$$V_2 = \frac{R_2}{(R_1 + R_2)} V_0$$

Capacitors

- A capacitor has capacity to store energy in the form of electrical charge producing a voltage across plates
- Storage of energy is time dependent
 - This was NOT the case in purely resistive circuits.
- Capacitance is measured in Farads [F]


$$i = C \frac{dV}{dt}$$

i = Instantaneous Current
 $\frac{dV}{dt}$ = Instantaneous rate of
 voltage change

$$C = \frac{\epsilon A}{d}$$

ϵ = dielectric constant
 A = Area of plate overlap
 d = distance between plates

Capacitors are
sometimes
polarized.

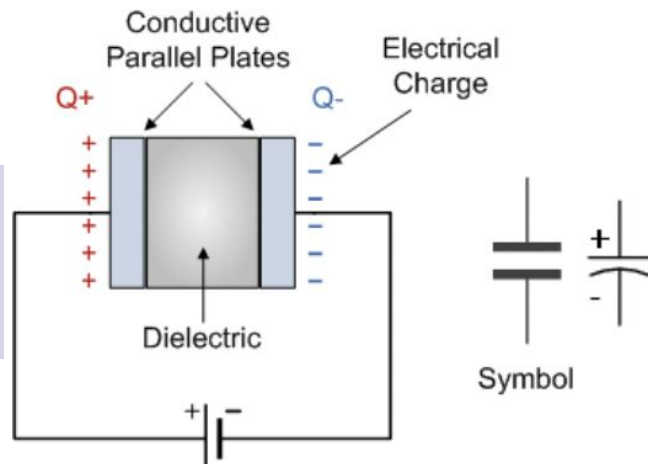

NOTE: Directly connecting a capacitor to a voltage supply is not practical.

Capacitors



- The charge on a capacitor cannot change instantaneously
- The charge on the plates of the capacitor is given as $Q = CV$
- The current flowing into a capacitor after a long time interval (i.e., steady-state) is zero
 - Charge contained in the capacitor instead of flowing through the circuit

RC Circuits

- RC circuits consist of a resistor and capacitor in series
- A capacitor stores energy and a resistor placed in series with it controls the rate at which it charges or discharges.



$$\tau \equiv RC$$

$$V_c = V_s(1 - e^{-t/\tau})$$

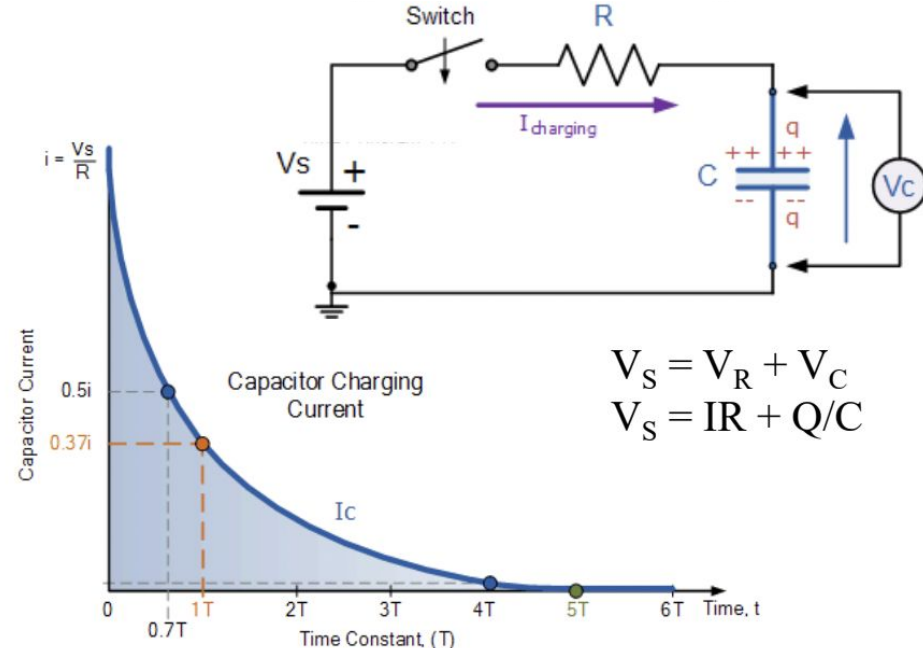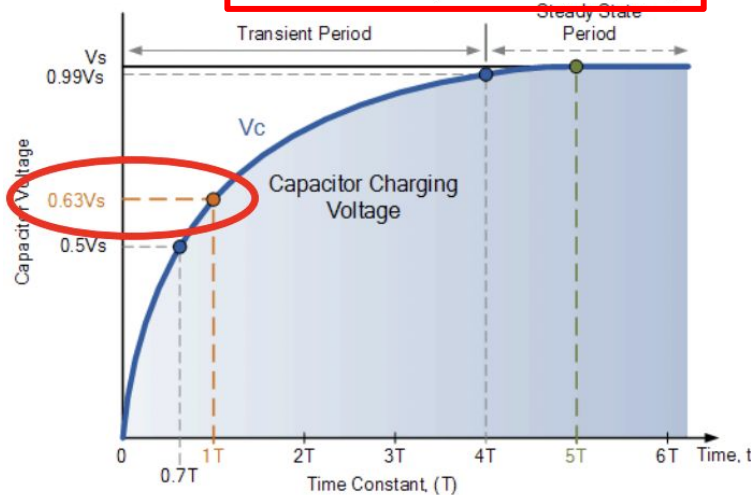


RC Circuits

Charge

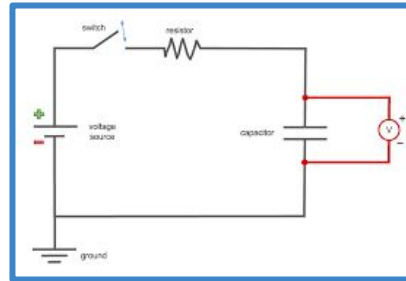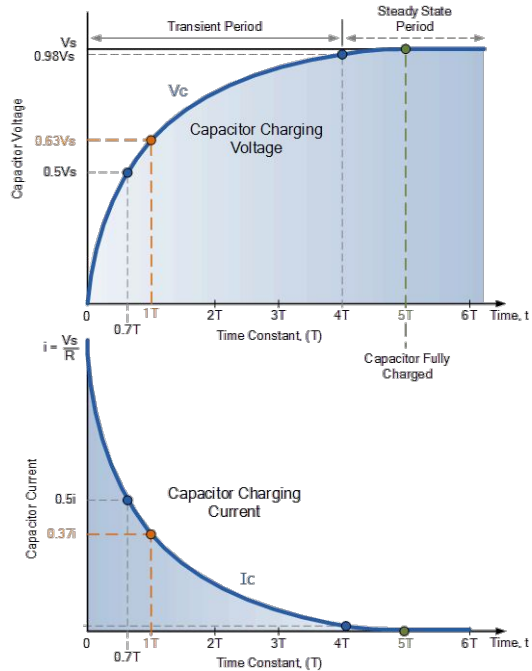

Discharge

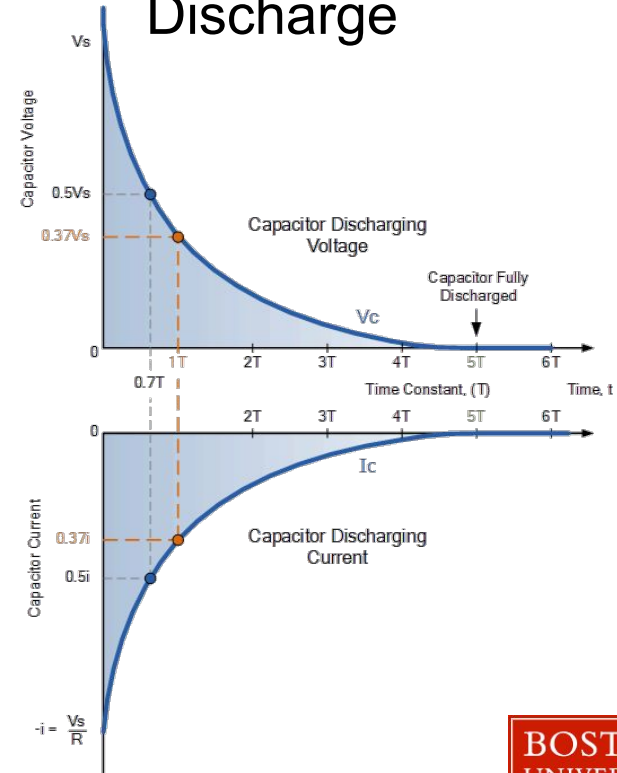

Experiment II

Resistor – Capacitor (RC) Circuits

Think – Pair – Share

