

MODULE 6: Photodiodes and VLC

BU SUMMER CHALLENGE
Electrical Engineering: Smart Lighting Project



Beste Oztop
PhD Student
Boston University
boztop@bu.edu

Overview

- Recap
- Photodiodes
- Integrated Circuits (ICs)
- Visible Light Communication
- Experiment
 - Photodiodes
 - Optical Channel
 - Optical Signaling

Recap - LED Drivers

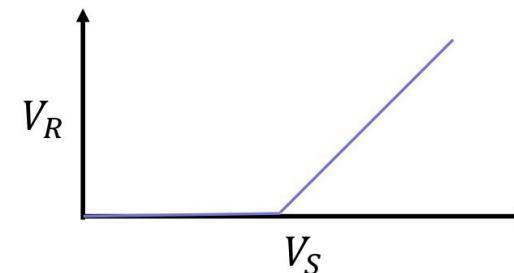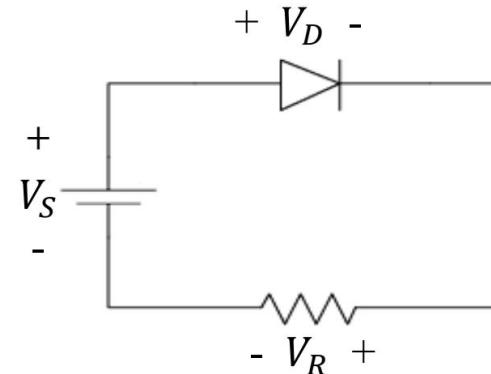- How does the VR relate to the current through the resistor?
- How does the current through the resistor relate to the current through the diode?
- What does the current through an LED relate to?




Recap - Electrical Power

- Power is the rate at which energy is consumed.
 - Voltage = Potential energy difference per unit charge [V] or [J/C]
 - Current = Rate of flow of charge [A] or [C/s]

$$P = VI$$

- Power is measured in Watts [W] or [J/s]
- Energy sources (such as batteries) produce power while the load of the circuit absorbs power.

Recap - Electrical Power

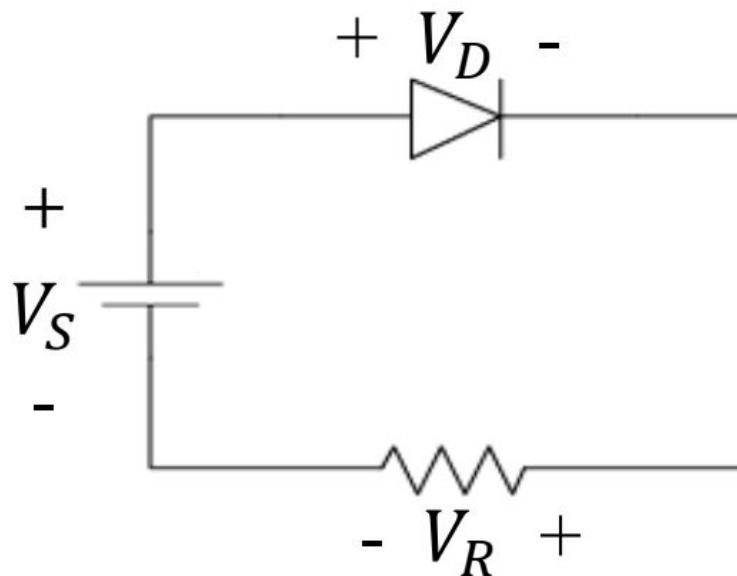


$$I = \frac{V_R}{R} = \frac{V_S - V_D}{R}$$

$$P_D = V_D I = \frac{V_D(V_S - V_D)}{R}$$

$$P_R = V_R I = \frac{(V_R)^2}{R} = I^2 R$$





Photodiodes

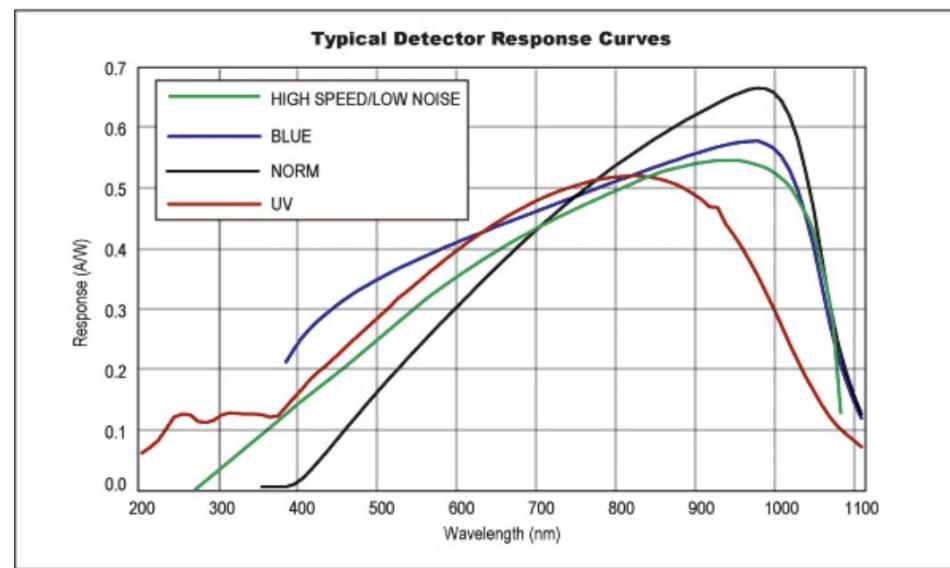- Current is generated proportional to the received optical power
- Responsivity [A/W] is a function of wavelength




Integrated Circuits (ICs)

- A collection of many electronic components connected together to carry out a common function
- E.g., circuit logic gates, computer memory, operational amplifiers (op-amps)

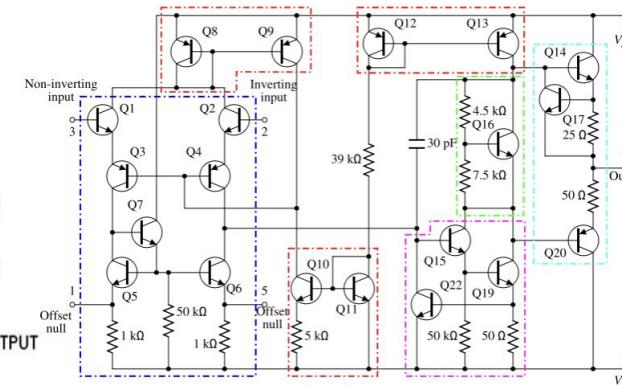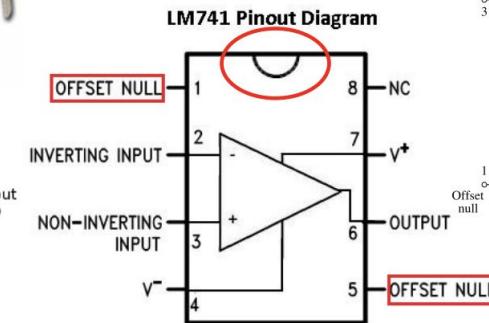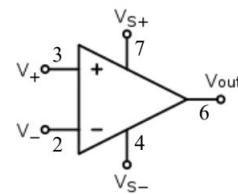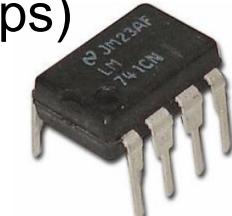


Experiment I

- Photodiode Circuit

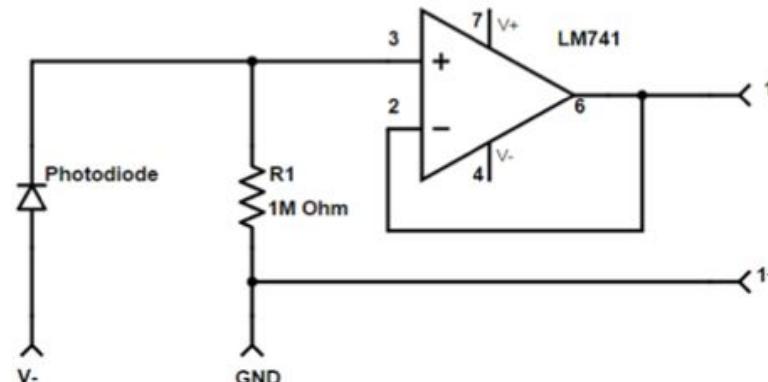

- Optical Channel

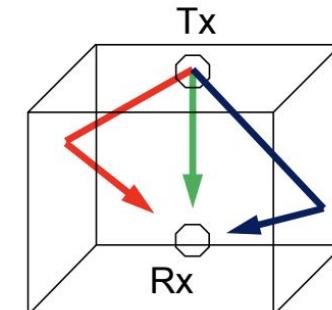- LEDs have an angle dependent emission pattern
- Photodiodes also have an angle dependent response
- Distance relates to signal attenuation
- Multipath attenuation adds time dispersion



Think – Pair – Share

WHAT?
did you
LEARN
today

An illustration of an open book with a magnifying glass resting on it, symbolizing learning and discovery.

Extra - Introduction to Arduino